

B.E. (EE) Part-III 5th Semester Examination, 2007

### Network Theory (EE-504)

Time : 3 hours

Full Marks : 100

Use separate answerscript for each half.  
Answer SIX questions, taking THREE from each half.  
Two marks are reserved for neatness in each half.

#### FIRST HALF

1. a) In the network shown in Fig.-1, N is a two port network. Find  $V_1$  and  $V_2$ .

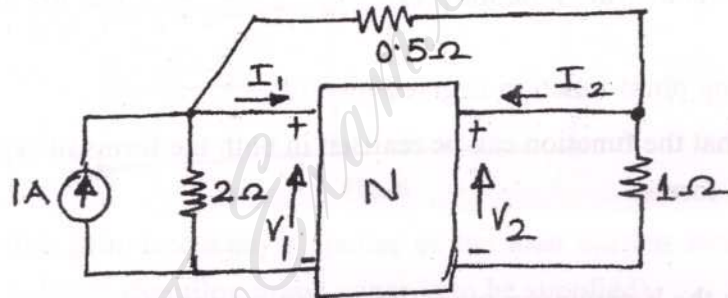


Fig.-1

- b) In Fig.-2 a RC network has been shown. Determine its ABCD parameters in Laplace domain. [8+8]

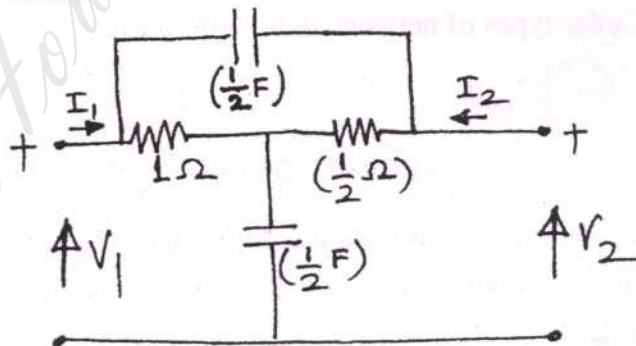


Fig.-2

2. a) Show that the overall ABCD parameters network matrix for a cascaded two port network is the matrix product of ABCD matrices of individual network.  
b) Explain briefly the concept of a ladder network. What is its utility?  
c) What are the types of negative converter? How would you model a negative converter for circuit analysis? [4+4+8]

(EE-504)

3. a) Which of the following networks shown in Fig.-3(a) and 3(b) does not have Z parameters? Why?

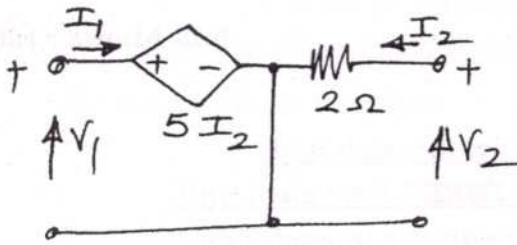


Fig.-3(a)

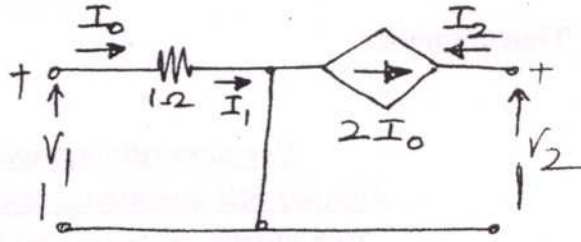


Fig.-3(b)

- b) Check whether the polynomial  $P(s)$  is Hurwitz, when  

$$P(s) = 4s^6 + 2s^5 + 17s^4 + 8s^3 + 16s^2 + 6s + 3$$
 [8+8]
4. a) Check whether the function  $Z(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$  is a PR function.
- b) A driving point function is given by  $F(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$ .  
 Show that the function can be realised in both the forms of type-1 Cauer RC and RL forms. [6+10]
5. a) Explain the h-parameter model of a two port network.
- b) The driving point impedance of a reactive network is given by  

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$
  
 Develop Cauer types of network in both the forms. [8+8]

**SECOND HALF**

6. a) Draw the oriented graph of the network of Fig.-4. Select a tree, from the Tie-set and Cut-set matrices. Solve for the branch voltages and branch currents by loop basis.

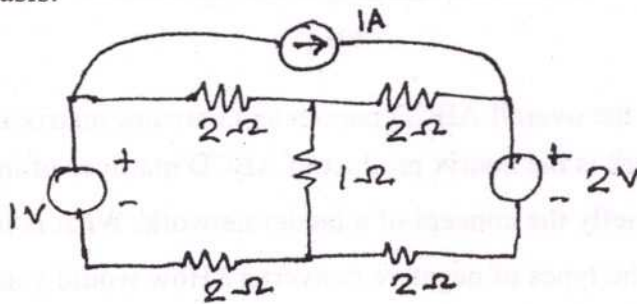


Fig.-4

- b) Define the 'Dual' and 'inverse' of a Network. Find the 'Dual' and 'inverse' of the network of Fig.-5. [10+6]

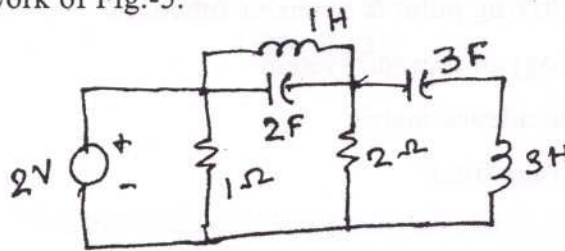


Fig.-5

7. a) Determine the driving point admittance ( $Y_{11}$ ) and transfer admittance ( $Y_{21}$ ) for the bridged T-network shown in Fig.-6 with  $2\Omega$  load resistor. Show the pole-zero plot of each network function.

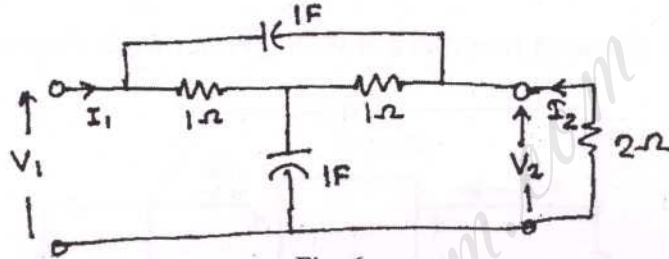


Fig.-6

- b) Draw the gain-frequency response of the load current with respect to the input voltage. (Semilog graph paper is to be supplied). [9+7]
8. a) Draw the electrical analogous circuit for the mechanical system shown in Fig.-7 using Force-current and Torque-current analogy.

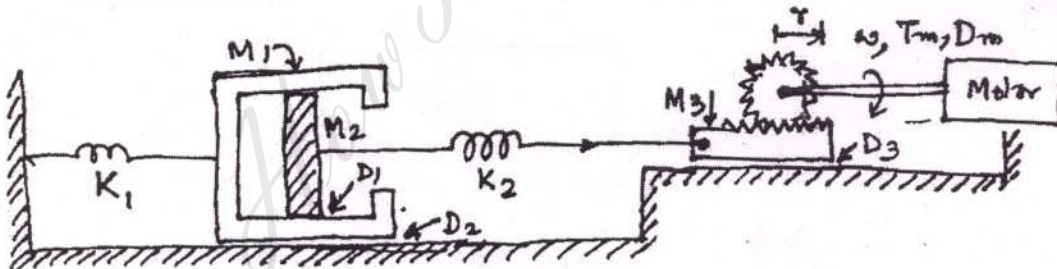


Fig.-7

- b) Draw the electrical analogous network for the interactive liquid level system. [12+4]
9. a) With the help of reactance diagrams, show the pass-band and stop-band gains of a prototype ions-pass filter.
- b) Design a prototype high-pass  $\pi$ -section filter having lower cut-off frequency of 1 kHz. Compute the filter parameters from fundamental principles. Assume a  $600\Omega$  load for the filter. [8+8]

(EE-504)

10. Write short notes on any two :

[8×2]

- a) Properties of driving point & Transfer functions
- b) Electrical analogy of thermal system
- c) Properties of incidence matrix
- d) Passive Band Pass filter.

-----

HowToExam.com