

B.E. (CST) Part-II 3rd Semester Examination, 2007

Digital Logic  
(CS-301)


Time : 3 hours

Full Marks : 70

Answer any FIVE questions, taking at least TWO from each group.

GROUP-A

 1. a) Draw the truth table for a Half-adder. Implement the half adder using logic gates.  
b) Draw the truth table of Full-adder and implement a 4-bit adder with half adders. Extra logic gates, if required, may be used. [7+7]




INPUTS				OUTPUTS			
SELECT	STROBE	DATA		1Y0	1Y1	1Y2	1Y3
B	A	1G	1C				
X	X	H	X	H	H	H	H
L	L	L	H	L	H	H	H
L	H	L	H	H	L	H	H
H	L	L	H	H	H	L	H
H	H	L	H	H	H	H	L
X	X	X	H	H	H	H	H

a) 74155 Pindigram

b) Function Table for 74155

Fig.-1 [Dual 1 of 4 decoder chip 74155]

 2. a) Implement full adder logic with dual 2-4 decoder (74155).  
b) Implement full adder logic with dual 4 to 1 line multiplexer (74153).  
For both the cases (i.e., (a) and (b)) list the number of IC-chips and extra gates necessary to implement 4-bit adders. [7+7]



SELECT		DATA INPUTS				STROBE	OUTPUT
B	A	C0	C1	C2	C3	G	Y
X	X	X	X	X	X	H	L
L	L	L	X	X	X	L	L
L	L	H	X	X	X	L	H
L	H	X	L	X	X	L	L
L	H	X	H	X	X	L	H
H	L	X	X	L	X	L	L
H	L	X	X	H	X	L	H
H	H	X	X	X	L	L	L
H	H	X	X	X	H	L	H

a) Pindigram

b) Function Table

Fig.-2 [Dual 4 to 1 multiplexer chip 74153]

(CS-301)

3. a) Design a combinational circuit using a ROM ( $8 \times 4$ ) that accepts a 3-bit binary number and produces the square of the corresponding input value. Note that the ROM has eight locations (i.e., 3-bit address) and 4-bit outputs and the square of a 3-bit number is to be expressed in 6 bits.
- b) Derive the program table for a combinational circuit to compute the square of a 3-bit number by using PLA. Minimize the number of product terms.

[7+7]

4. a) Design the sequential circuit, whose state table is given below, using a 2-bit register and combinational gates.


Present State		Input	Next State	
A	B	x	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	0	1

- b) Draw the circuit for a 4-bit bidirectional shift register with parallel load facility. The shift register should have clear and clock inputs as well as two mode control ( $s_1$  and  $s_0$ ) inputs.

[7+7]


### GROUP-B

 5. a) Which logic level limits the fan-out of a TTL gate and why?
- b) The output of a DTL inverter is connected to other N number of similar gates. Assume that the output transistor is saturated and  $h_{FE}$  of the output transistor is 30. Find the value of N that will keep the transistor in saturation.
- c) Compare TTL and CMOS logic families.
6. a) The following logic diagram is used to describe a sequential machine. Draw the state diagram depending on the assumed initial state.



(CS-301)

 - b) Design a 3-bit modulo-6 gray code counter with up/down capability using J-K flip flops.
  - c) Design a 16:1 MUX using 4:1 MUXs. [5+5+4]
7. a) Determine the logic function for the following circuit and explain its operation.



- b) Use open collector inverter gates to realize the two input exclusive OR function.
- c) Define Moore machine and Mealy machine. [6+4+4]
8. a) Why can't you make  $S=1$  and  $R=1$  in an RS flip-flop? Describe the Race-around problem in level triggered J-K flip-flop.
- b) A serial adder uses 2 shift registers and a flip flop. Draw the logic diagram and explain its operation. [(4+4)+6]