

B.E. (CST) Part-II 4th Semester Examination, 2006

### Network and Transmission Lines

(EE-407)

Time : 3 hours

Full Marks : 100

Use separate answerscript for each half.  
Answer SIX questions taken THREE from each half.  
Two marks are reserved for neatness in each half.

#### FIRST HALF

1. a) From the definition of Laplace transformation, prove that:

—

where all symbols carry their usual meanings. b) Obtain Laplace transform of the rectangular pulse shown in Fig. 1.

9+7

**JW**  
/0

T,

Fig.1

2. a) State and prove the Initial value and Final value theorems in Laplace transformation.

b)

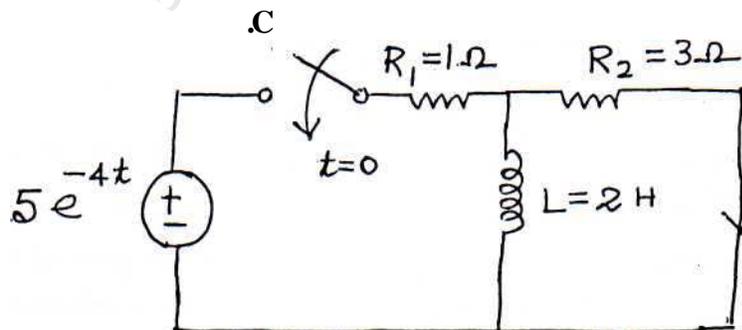


Fig.2

The circuit shown in Fig.2 was initially at rest. The switch S is suddenly closed at  $t = 0$ . Determine the current  $i_2(t)$  using Laplace transformation.

8+8

3. a) State and prove the Time Shift theorem in Laplace transformation.

(EE-407)

— (2) —

- b) A rectangular pulse of 2 sec. duration as shown in Fig.3(a) is applied to the circuit of Fig.3(b), which was initially at rest, at  $t=0$ . Using Laplace transformation method find out the voltage  $V_c(t)$  across the capacitor and sketch the wave form.

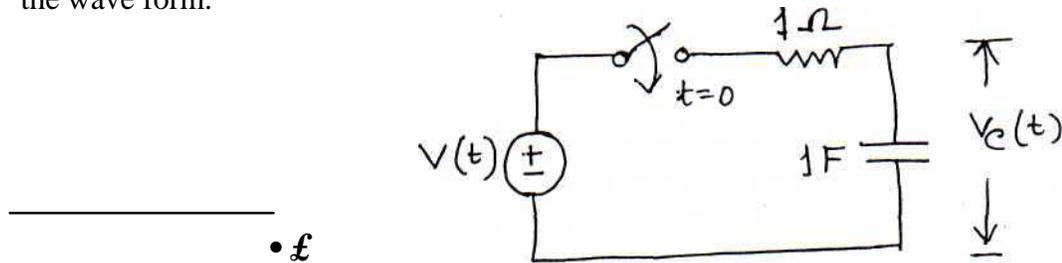


Fig.3

7+9

4. a) What is the characteristic impedance of a filter? Obtain the characteristic impedance for a prototype T-type filter in terms of reactance values of the filter arms.
- b) What is cut-off frequency of a filter? Derive the expression for cut-off frequency for a prototype low pass filter. 8+8
- 
- a) What is attenuation constant ( $\alpha$ ) and phase shift constant ( $P$ ) of a filter?
- b) Derive the expressions for attenuation and phase shift in a prototype high pass filter in its pass band and attenuation band. 6+10

### SECOND HALF

6. a) Derive an expression for characteristic impedance of a transmission line. How does the expression for it change when the line is lossless?
- b) Derive an expression relating the propagation constant with primary constants of a transmission line.
- c) Write down expressions for current and voltage at any point at a distance "x" from the sending end of a line using "Line Equations" (derivation not needed) and obtain the values of constants used in line equations when the conditions at the sending end are known.
- d) Assuming the expressions for "line equations" obtain the value of the input impedance of a line in terms of exponential form (derivation of line equations not needed). 4x4

(EE-407)

(3)

7. a) Calculate the primary constants of a transmission line having  $(Z_0) = 710 \angle -14.24^\circ$  ohm and  $y(\gamma) = 0.0185 \angle 74.81^\circ$  at  $f = 1$  kHz.
- b) The permissible approximations for unloaded underground cable at audio frequency are  $\omega C \gg G$  and  $\omega L \ll R$ . Calculate the characteristic impedance, attenuation and phase constants. Also find the velocity of propagation.
- c) Analytically establish the characteristics of a high frequency transmission line. 6+6+4
8. a) What is reflection coefficient? Derive a relation between the reflection coefficient and voltage standing wave ratio.
- b) A section of HF lossless transmission line is  $(0.4\lambda)$  long and is terminated in a short circuit the characteristic impedance of the line is 73 ohms; determine the input impedance of the line section at operating frequency of 200 MHz. Deduce the necessary formula used.
- c) Derive the expression of the reactance to be inserted in an ordinary shunt equalizer. What is its use? 4+8+4
9. a) A pair of two port networks are connected in cascade. Show that the overall ABCD parameter network matrix is the matrix product of ABCD parameter matrices of individual networks. \_\_\_\_\_
- b) Obtain the expressions of input and output impedances of a two port network in terms of transmission parameters.
- c) Find Z-parameters of a lattice network assuming the series arm impedance to be  $Z_1$  ohm (each) while the diagonal impedance is  $Z_2$  ohm (each). 5+5+6
10. a) Write short notes on (any two) : i) Concept of inverse network ii) Stub matching in transmission line iii) Loading of lines
- b) The currents  $I_1$  and  $I_2$  at input and output port unsymmetrical two port network ("pi" configuration) is expressed as  $I_1 = 5V_1 - V_2$  and  $I_2 = -V_2 + V_1$ . Assuming  $Y_1$  and  $Y_2$  to be the shunt arm admittances while  $Y_3$  is the series arm admittance of the "pi" network, find the values of  $Y_1$ ,  $Y_2$  and  $Y_3$ . Find also the input impedance of the given circuit when a load of  $(3 + j5)$  ohms is connected across the output port. 4 x 2+8