

Register Number :

Name of the Candidate :

6 1 2 0

B.E. DEGREE EXAMINATION, 2008

(COMPUTER SCIENCE AND ENGINEERING)

(FOURTH SEMESTER)

**COEC - 401. ELECTRONIC CIRCUITS
AND SYSTEMS**

May]

[Time : 3 Hours

Maximum : 60 Marks

Answer any ONE full question from each unit.

UNIT - I

1. (a) What is meant by PIV rating of a diode ?
What is its importance ? (4)
- (b) Explain the operation of a bridge rectifier.
Also, derive an expression for rectification
efficiency and Transformer utility factor.(8)
2. (a) Compare series and shunt type voltage
regulators. (3)

Turn over

- (b) With a suitable diagram, explain the operation of a switched mode regulator. (9)

UNIT – II

3. (a) What is a Darlington pair amplifier ? (3)
(b) Explain the operation of a transformer coupled amplifier. (9)
4. (a) Distinguish CLASS-A from CLASS-B amplifiers. (3)
(b) Derive expressions for power dissipation and conversion efficiency of a CLASS-A push-pull amplifier. (9)

UNIT – III

5. (a) Define the term 'Input offset current' of an OP-AMP. (3)
(b) Suggest a suitable technique for Input offset current in an OP-AMP. Explain its operation. (9)
6. (a) Draw the circuit of an OP-AMP based V to I converter. (4)

- (b) Draw the circuit of an OP-AMP peat detector and explain its operation. (8)

UNIT – IV

7. (a) Draw and explain the operation of an OP-AMP based Schmidt Trigger. (9)
(b) State the applications of a zero crossing detector. (3)
8. (a) Define Lock – in range and capture range of a PLL. (4)
(b) Explain the astable operation of a 555 Timer with necessary circuit diagram and waveforms. (8)

UNIT – V

9. (a) How an inverted R-2R ladder type DAC differs from simple R-2R ladder type DAC. (3)
(b) With suitable diagrams, explain the operation of an inverted R-2R Ladder type DAC. (9)

10. (a) What is the conversion time and resolution of an 8 bit successive approximation type ADC driven by a 1 MHz Clock. The internal reference voltage is 5V. (4)

(b) Explain the operation of a dual slope ADC. (8)