



Printed Pages : 7

TEE – 402

(Following Paper ID and Roll No. to be filled in your Answer Book)	
PAPER ID : 2052	Roll No. <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/> <input style="width: 20px; height: 20px;" type="text"/>

B. Tech.

(SEM. III) EXAMINATION, 2006-07

NETWORK ANALYSIS & SYNTHESIS

Time : 3 Hours]

[Total Marks : 100

Note : Answer *all* questions. All questions carry equal marks.

1 Attempt any **three** parts of the following : $6\frac{2}{3} \times 3 = 20$

(a) Using graph theory, find node voltages at X and Y for the network shown in **Fig. 1 (a)**

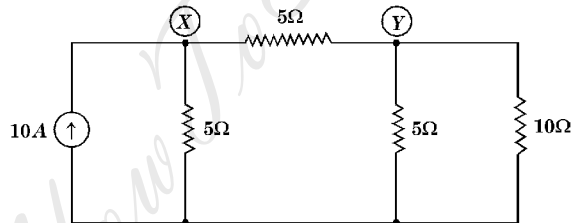


Fig. 1 (a)

(b) Write down the fundamental loop matrix of the network shown in **Fig. 1 (b)**.

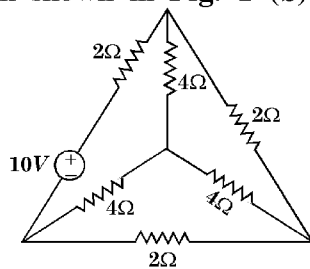


Fig. 1 (b)

V-2052]

[Contd...

- (c) In graph theory, determine the relation between branch voltage matrix $[V_o]$, Twing voltage matrix $[V_T]$ and node voltage matrix $[V_n]$.
- (d) Draw the oriented graph of a network with fundamental outset matrix as shown below:

<i>Twings</i>				<i>Links</i>		
1	2	3	4	5	6	7
1	0	0	0	-1	0	0
0	1	0	0	1	0	1
0	0	1	0	0	1	1
0	0	0	1	0	1	0

Also find no. of fundamental outset and draw them.

- (e) Using graph theory prove that two given networks in **Fig. 1 (e) (i)** and **1 (e) (ii)** are duals to each other.

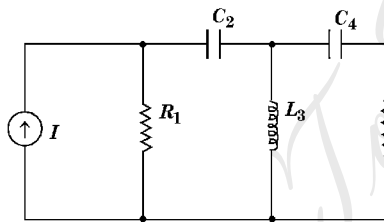


Fig. 1 (e) (i)

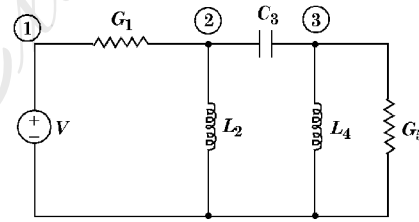


Fig. 1 (e) (ii)

2 Attempt any **three** parts of the following : **62/3x3=20**

- (a) Find Voltage ' v ' using superposition theorem of the network shown in **fig. 2 (a)**.

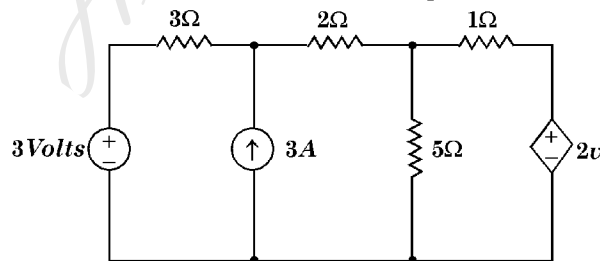


Fig. 2 (a)

V-2052]

[Contd...

- (b) Find the Norton's equivalent for the network given in **fig. 2(b)** across A and B.

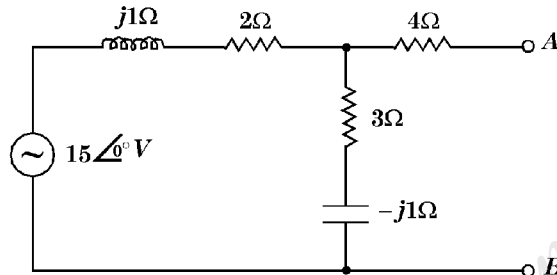


Fig. 2 (b)

- (c) Determine the value of Z_L for which it receives maximum power and calculate this power of the network shown in **fig. 2 (c)**.

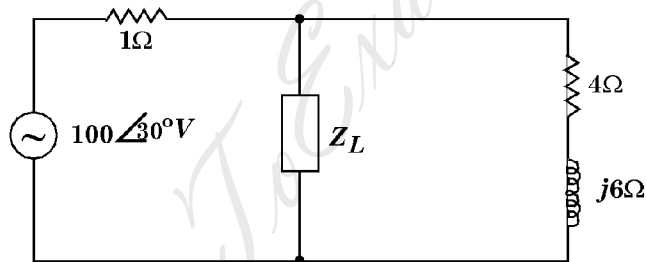


Fig. 2 (c)

- (d) State Millman's theorem for voltage and current sources. Also find the current through R_L in the network shown in **fig. 2 (d)** using millman's theorem.

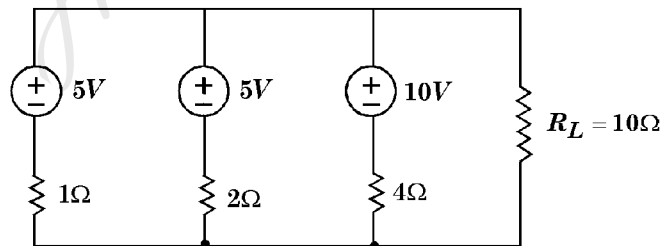


Fig. 2 (d)

V-2052]

[Contd..

- (e) State compensation theorem. Find the change in current flowing through the impedance Z , when its value is changed from $(4-j3) \Omega$ to $(6+j8) \Omega$ using it in the network shown in **fig. 2 (e)**.

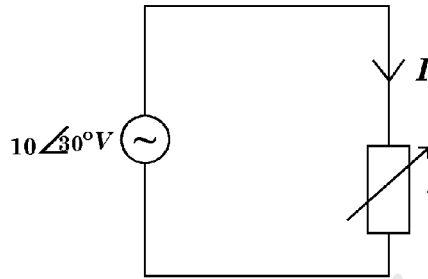


Fig. 2 (e)

3 Attempt any **two** parts of the following : **10×2=20**

- (a) Enlist the restrictions on location of poles and zeros in driving point function.

In the network of **fig. 3 (a)**, find $\frac{V_c(s)}{V(s)}$.

Also find the pole zero locations and draw pole-zero plate of it.

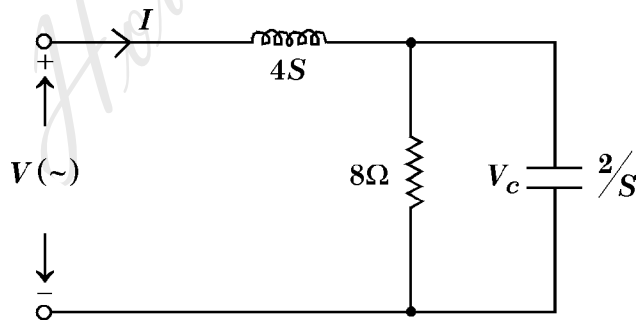


Fig. 3 (a)

V-2052]

[Contd..

- (b) Obtain $V_2(s)/V_1(s)$ of the network shown in **fig. 3 (b)**

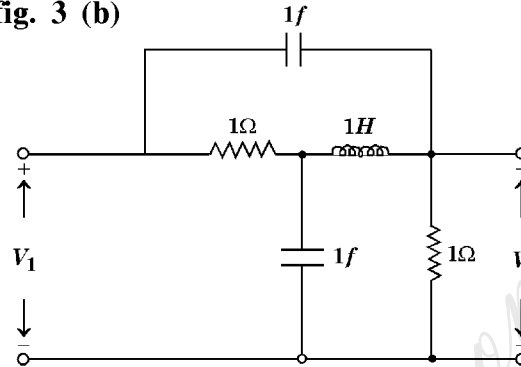


Fig. 3 (b)

- (c) How can stability of the network be obtained with the help of pole-zero plot. Determine driving point impedance function of the network shown in **fig. 3(c)**. Draw pole-zero plot and discuss stability of the network.

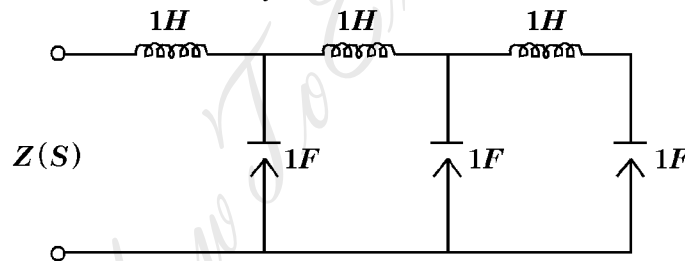


Fig. 3(c)

- 4 Attempt any **two** parts of the following : **10×2=20**

- (a) Obtain Z-parameters of the network shown in **fig. 4 (a)**. Whether the network is reciprocal and/or symmetrical.

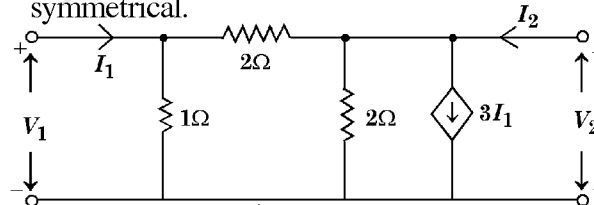


Fig. 4 (a)

V-2052]

[Contd..

- (b) Determine the h-parameters of the network shown in **fig. 4 (b)**.

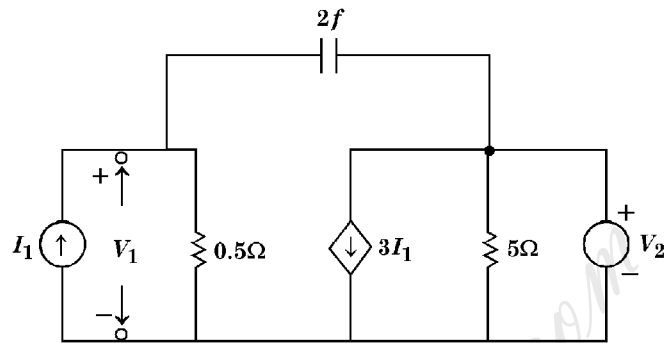


Fig. 4 (b)

- (c) Determine Y-parameters of two port network shown in **fig. 4 (c)** using interconnection principle.

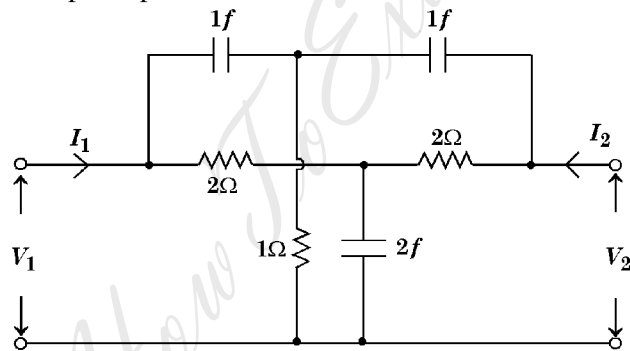


Fig. 4 (c)

5 Attempt any **three** parts of the following : $6 \frac{2}{3} \times 3 = 20$

- (a) Design the T and π section of a prototype high pass filter having cut-off frequency of 20 kHz and design impedance of 450 ohms. Also find its characteristic impedance and phase constant at 25 kHz as well as determine the attenuation at 4 kHz.

V-2052]

6

[Contd..

- (b) In a series resonance type band pass filter, $L = 60 \text{ MH}$, $C = 150 \text{ nf}$ and $R = 70 \text{ ohms}$. Determine (i) resonance frequency in HZ, (ii) Bandwidth (iii) cut-off frequencies. Assume the load resistance to be 600 ohms .

- (c) Explain the advantages of active filters in comparison to passive filters.

An admittance function is given as

$$y(s) = \frac{4s^2 + 6s}{s + 1}$$

Realise the network using Caver's first and second form.

- (d) Enlist the properties of driving point immittance of LC network.

State whether the following functions are driving point immittances of LC network or not:

(i) $Z(s) = \frac{10(s^2 + 4)(s^2 + 6)}{(s^2 + 1)(s^2 + s)}$

(ii) $z(s) = \frac{5s(s^2 + 4)}{(s^2 + 1)(s^2 + 3)}$

(iii) $z(s) = \frac{8(s^2 - 4)(s^2 + 25)}{s(s^2 + 16)}$

- (e) An impedance function at the input of a network is represented by

$$z(s) = \frac{(s^2 + 5s + 4)}{(s^2 + 2s)}$$

Express it in the second faster form.