

Roll No.....

Total No. of Questions : 13]

[Total No. of Pages : 02

Paper ID [A0305]

(Please fill this Paper ID in OMR Sheet)

B.Sc. IT/DCA (201) (S05) (N) (Sem. - 2nd)

DIGITAL ELECTRONICS FUNDAMENTALS

Time : 03 Hours

Maximum Marks : 75

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Nine** questions from Section - B.

Section - A

Q1)

(15 × 2 = 30)

- a) Convert the following hexadecimal numbers into decimal
 - (i) 3FFE
 - (ii) 2180
- b) (10101) convert to Decimal Number system.
- c) How subtraction of 4-bit no. is performed by addition?
- d) Using Boolean algebra simplify following expression
A. $(B+B'C)$
- e) Represent (-17) decimal number into 1's complement and 2's complement form.
- f) Draw and give truth table for EX-OR gate.
- g) Write the working of 4: 1 multiplexer.
- h) Give working of half adder.
- i) Explain NOR gate with truth table.
- j) Draw circuit for full subtractor.
- k) Give the advantages of edge triggered flip-flops.
- l) What is a race around condition?
- m) Differentiate between volatile and non-volatile memory.
- n) What is Flip-flop?
- o) Draw and give truth table for D flip flop.

A-280

P.T.O.

Section - B

(9 × 5 = 45)

- Q2)** Draw the minimized logic circuit for the Boolean equation
$$Y = A'B'C'D + AB'C'D + ABC'D + ABCD'$$
- Q3)** Convert decimal no. 100.55 into binary, octal codes.
- Q4)** State and discuss the De-Morgan's Theorem's.
- Q5)** Write expression for Boolean function $F(A,B,C) = \sum m(1,4,5,6,7)$ in standard POS form.
- Q6)** How are AND, OR and NOT operations realized with NAND gates?
- Q7)** Draw the circuit of a 3 to 8 decoder and explain its operation.
- Q8)** Draw and explain full adder using two multiplexers.
- Q9)** Draw and explain Decimal to binary encoder.
- Q10)** Discuss the working of JK master slave flip-flop.
- Q11)** Give relative merits for storing data in ROM, PROM and EPROM.
- Q12)** Draw and explain S-R flip flop using NAND gate.
- Q13)** Explain magnetic and semiconductor memory.

