

THAPAR INSTITUTE OF ENGINEERING AND TECHNOLOGY, PATIALA
END SEM EXAM (JULY-DEC 06)
B.E. FIRST YEAR (D, E, F Group)

Subject: Electrical and Electronics Science (ES-101)

Time: 3 hr

Max. Marks: 72

NOTE: Attempt any five questions. Question 1 is compulsory.

Attempt questions in sequence. Write group number on top of the sheet.

- 1.a Draw and explain the input & output characteristics of CB transistor. (5)
- 1.b Determine the output voltage waveform for the network of fig 1. (5)
- 1.c Discuss the Barkhausen criterion for oscillator. (5)
- 1.d Explain the working of FET or MOSFET and how it is different from BJT. (5)
- 1.e Give any eight energy saving tips to a housewife. (4)

- 2.a Draw and explain the operating characteristics of D.C. series and shunt motor. (6)
- 2.b Use THEVENIN'S theorem to calculate the current passes through 3-ohm resistor of the circuit shown in fig 2. (6)

- 3.a A 230V D.C. series motor has an armature circuit resistance of 0.2 ohm and field resistance of 0.1 ohm. At rated voltage the motor draws a line current of 40A and runs at a speed of 1000 r.p.m. Find the speed of the motor for a line current of 20A at 230V. Assume that the flux at 20A line current is 60% of the flux at 40A line current. (6)
- 3.b Find the voltage drop across 3-ohm resistor using nodal analysis of the circuit shown in fig 3. (6)

- 4.a Explain the working principle of 1-phase induction motor and also give any two types of it along with their circuit diagram. (6)
- 4.b For the zener diode network of fig 4, determine V_L , V_R and I_Z . (6)

- 5.a Derive the relationship of air gap power for 3-phase induction motor. (6)
- 5.b Calculate the total power input and readings of the two wattmeter connected to measure power in a three phase balanced load; if the reactive power input is 15KVAR and load power factor is 0.8 lag. (6)

- 6.a A ring of cast steel has an external diameter of 24 cm and a cross-section in the form of square of 3 cm side as shown in fig 5. Inside and across the ring a cast steel bar of 18cm×4cm×0.3cm is fitted with negligible air gap. Calculate the number of Ampere-turns to be applied to the half of the ring to produce a flux density of 1 Wb/m² in the other half. Neglect leakage, magnetization curve of the cast steel is as following:

B (Wb/m ²):	0.2	0.4	0.6	0.9	1.0	1.07	1.1765	1.325
H (AT/m):	300	460	600	800	900	1000	1200	1650

(6)

P.T.O.

- 6.b A 200 KVA transformer has an efficiency of 98% at full load. If the maximum efficiency occurs at three-quarter of full load, calculate the efficiency at half load. Assume negligible magnetizing current and power factor of 0.8 at all loads. (6)

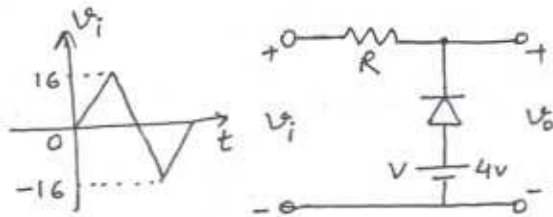


Fig 1

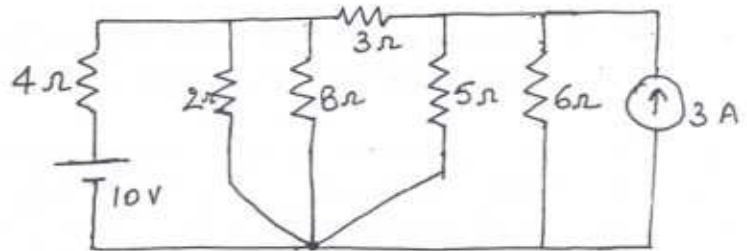


Fig 2

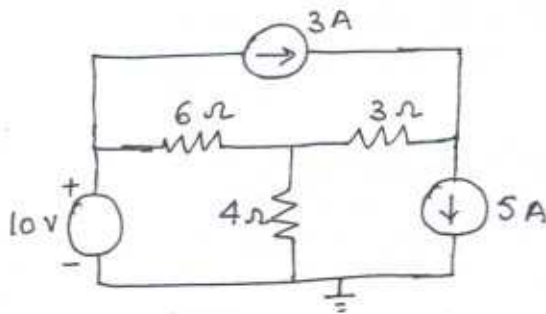


Fig 3

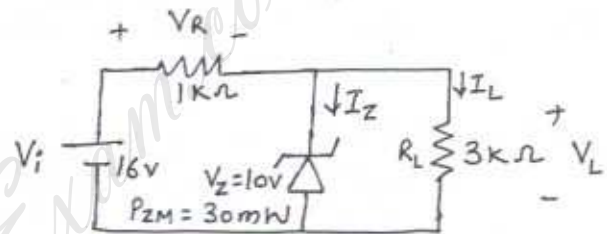


Fig 4

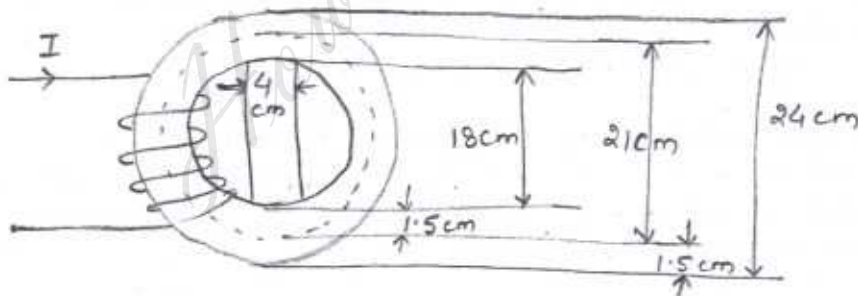


Fig 5

NOTE: Students can see their evaluated answer sheet on 15/12/06 as per the following schedule:

GROUP	TIME	ROOM
D	12 noon	D-115
E	12:45 p.m.	D-115
F	1:30 p.m.	D-115