

Total No. of Questions : 12]

[Total No. of Printed Pages : 4

**[3861]-154**

**F. E. (Semester - I) Examination - 2010**

**BASIC ELECTRICAL ENGINEERING**

**(2008 Pattern)**

**Time : 3 Hours]**

**[Max. Marks : 100**

**Instructions :**

- (1) *Answers to the two sections should be written in separate answer-books.*
- (2) *Answer Q. No. 1 or Q. No. 2, Q. NO. 3 or Q. No. 4, Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8, Q. No. 9 or Q. No. 10 and Q. No. 11 or Q. No. 12.*
- (3) *Figures to the right indicate full marks.*
- (4) *Neat diagrams must be drawn wherever necessary.*
- (5) *Use of non-programmable pocket size scientific calculator is permitted.*
- (6) *Assume suitable additional data, if necessary.*

---

---

**SECTION - I**

- Q.1)** (A) What is Insulation Resistance ? State its unit and obtain an expression for Insulation Resistance of the Cable. **[08]**
- (B) With neat sketch explain Construction and Working of Lead Acid Cell. **[08]**

**OR**

- Q.2)** (A) A resistance element having cross-sectional area of 10 mm<sup>2</sup> and length of 10 meter takes a current of 4 Amp from 200V supply at temperature of 25°C. Find (i) resistivity of the material and (ii) current it will take when temperature rises to 75°C. Assume  $\alpha_{25} = .0003/^{\circ}\text{C}$ . **[06]**

**[3861]-154**

**1**

**P.T.O.**

- (B) If  $\alpha_1$  and  $\alpha_2$  are the two resistance temperature coefficients at  $t_1$  °C and  $t_2$  °C, then prove that  $(\alpha_1 - \alpha_2) = \alpha_1 \alpha_2 (t_2 - t_1)$ . [06]
- (C) State applications of Nickel-Iron Cell and Nickel-Cadmium Cell. [04]

- Q.3)** (A) State and explain Superposition Theorem as applied to Simple DC Circuit. [06]
- (B) State and explain Kirchoff's Laws. [04]
- (C) Determine resistance between (x) and (y) for the circuit shown in fig. 1 : [06]

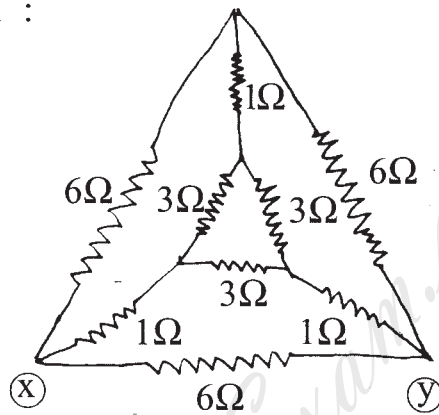


Fig. 1

OR

- Q.4)** (A) State and explain Maximum Power Transfer Theorem. [06]
- (B) Apply Thevenin's Theorem to the circuit show in fig. 2 to calculate current in  $01\Omega$  resistance : [10]

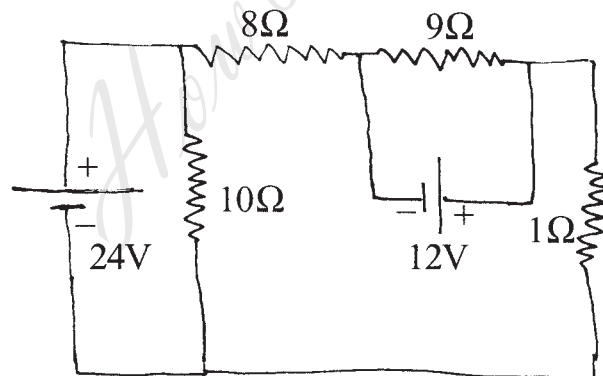


Fig. 2

- Q.5)** (A) Compare Electric and Magnetic Circuit. [08]
- (B) Write short notes : [10]
- (a) Magnetic Leakage and Fringing.
  - (b) Energy stored in a Magnetic Field.

OR

- Q.6)** (A) Explain what do you mean by Statically Induced emf and Dynamically Induced emf ? [06]
- (B) A steel ring of 25 cm mean diameter and of circular cross-section 3 cm diameter has an air gap of 1.5 mm length. It is wound uniformly with 700 turns of wire carrying a current of 2 Amp. Calculate :
- (a) MMF
  - (b) Flux Density
  - (c) Reluctance and
  - (d) Relative Permeability of Steel Ring [12]

**SECTION - II**

- Q.7)** (A) Define w.r.t. alternating quantities : [09]
- (a) Instantaneous Value
  - (b) Waveform
  - (c) Cycle
  - (d) Amplitude
  - (e) Periodic Time
  - (f) Frequency
- (B) Sketch Waveforms of Currents and find its rms value and average value for the equation : [08]
- (a)  $i_1 = 15 \sin (314.159 t)$  and
  - (b)  $i_2 = 10 \sin (314.159 t - \pi/2)$

**OR**

- Q.8)** (A) Prove that rms value of the sinusoidal alternating current is 0.707 times its maximum value. [06]
- (B) Derive expression for energy stored in a capacitor. [06]
- (C) Two capacitors of  $50\mu\text{F}$  each are connected in parallel with each other and this combination is connected in series with two capacitors of  $80\mu\text{F}$  of  $40\mu\text{F}$  each. Calculate equivalent capacitance of the circuit. [05]

- Q.9) (A)** Define and explain following terms : **[08]**
- (a) Active Power
  - (b) Reactive Power
  - (c) Impedance
  - (d) Admittance

- (B)** A Circuit consisting of Resistance of  $20\Omega$  and Inductance of  $0.1$  Henry is connected in series across single phase  $200V$ ,  $50$  Hz supply. Calculate :
- (a) Current Drawn
  - (b) Power Consumed
  - (c) Draw relevant Phasor Diagram **[09]**

**OR**

- Q.10) (A)** A Coil of Resistance  $50\Omega$  and Inductance of  $0.1$  H is connected in parallel with a branch which consists of resistance of  $45\Omega$  in series with a capacitor of  $100\ \mu F$  across a single phase  $230V$ ,  $50Hz$  supply. Calculate Current, Power and p.f. of the Circuit. **[09]**

- (B)** If a sinusoidal voltage of  $v = V_m \sin \omega t$  is applied across R-C series circuit, derive expression for current drawn and power consumed. Draw their waveforms also. **[08]**

- Q.11) (A)** Write short notes : **[08]**
- (a) Losses taking place in Transformer
  - (b) An Autotransformer

- (B)** Draw a complete phasor diagram for a 3 phase delta connected inductive balanced load supplied for 3-phase symmetrical A.C. supply. State equation for Active Power and Reactive Power consumed by Load. **[08]**

**OR**

- Q.12) (A)** A balanced Star Connected Load is supplied by 3-phase,  $415V$ ,  $50Hz$  supply. Current in phase is  $20$  Amp and lags  $30^\circ$  behind its phase voltage. Find :
- (a) Power Consumed by Load
  - (b) Circuit Parameters, and
  - (c) Load p.f. **[08]**

- (B)** Explain working principle of transformer and derive expression for emf induced in its winding. **[08]**

---

**[3861]-154/4**