



\* R N - 6 1 2 5 / 2 0 0 \*

**RN-6125**

**B. E. - II (Sem. III) (Chemical) Examination**

**May / June - 2010**

**Basic Electronics**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दर्शाविएव निशानीवाणी विगतो उत्तरवडी पर अवश्य वजवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<b>B. E. - 2 (Sem. 3) (Chemical)</b>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<b>Basic Electronics</b>	<input type="text"/>
Subject Code No. : <input type="text"/> 6 <input type="text"/> 1 <input type="text"/> 2 <input type="text"/> 5	Section No. (1, 2,....) : <input type="text"/> 1&2
Student's Signature	

- (2) Attempt all questions.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data wherever necessary and specify your assumption clearly.

- 1 (a) Answer the following : 10
- (i) A bridge type rectifier has \_\_\_\_\_ diodes.
  - (ii) A pentavalent impurity has \_\_\_\_\_ valence electrons.
  - (iii) Define :
    - (a) PIV
    - (b) Filters
    - (c) Cut in voltage
  - (iv) At room temperature, an intrinsic semiconductor acts as \_\_\_\_\_.
  - (v) A zener diode is used as a \_\_\_\_\_.
  - (vi) The ripple factor of a half wave rectifier is \_\_\_\_\_.
  - (vii) The relation between B and D is \_\_\_\_\_.
  - (viii) In a transistor, signal is transferred from a \_\_\_\_\_ circuit.
- (b) Explain half wave rectifier and derive equation for its efficiency. 6
- (c) Define filter and compare various filters. 4

- 2 (a) Explain with the help of neat diagram transistor working as an amplifier. 8
- (b) Describe with the characteristics, the voltage stabilization of zener diode. 7
- OR**
- 2 (a) Define biasing of transistor. List the various methods of biasing and explain voltage divider biasing. 8
- (b) Describe the working of following filters 7
- (i) Capacitive filter
- (ii)  $\pi$  filter.
- 3 Write short notes on : (any three) 15
- (i) Comparison of CE, CB, CC configuration of transistor.
- (ii) Classification of amplifiers
- (iii) Uni-junction transistor
- (iv) Push pull amplifier.


### SECTION - II

- 4 (a) (i) An astable multivibrator \_\_\_\_\_ 1
- (a) Gives one output pulse for every two input pulse.
- (b) Give a timed output pulse for trigger input.
- (c) Gives a train of output pulses for trigger input.
- (d) Gives four output pulses for single input pulse.
- (ii) The electrons emitted by a thermionic emitter are called \_\_\_\_\_. 1
- (a) Free electron
- (b) Loose electron
- (c) Thermionic electron
- (d) Bound electron
- (iii) In signal generators energy is converted from simple \_\_\_\_\_ source into \_\_\_\_\_ energy at some specific frequency. 2
- (iv) Define work function. 2
- (v) What is full form of LED? 2
- (vi) What is deflection sensitivity of CRT? 2
- (b) (i) List various devices used for measurement of temperature. 4
- (ii) What is field emission? 3
- (iii) Give merits and demerits of multimeter. 3

- 5 (a) What is secondary Emission? Explain with labelled diagram. 7  
 (b) Explain function of internal parts of CRT with diagram. 8

OR

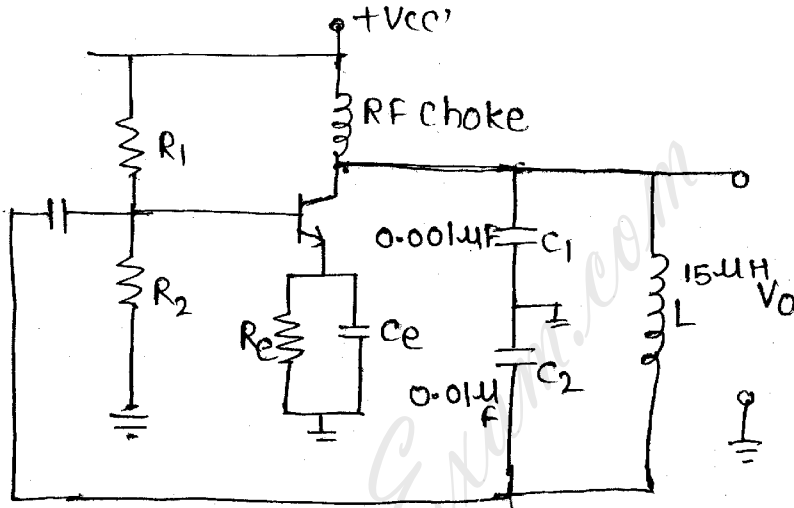- 5 (a) Determine frequency of oscillation and feedback fraction for colpitts oscillator. 8  
 Given  $C_1 = 0.001$  Micro Faeade,  $C_2 = 0.01$  Micro faeade  
 $L = 15$  Micro henry



- (b) Explain Barkhausen criteria with neat block diagram. 7
- 6 Any three : 15  
 (i) Explain frequency measurement using CRO. 5  
 (ii) What is Photo Electric emission? Explain with diagram. 5  
 (iii) Write about Thermionic Emitter. 5  
 (iv) Write a note on photodiode with characteristics. 5