



SB-0716

Second Year B. Sc. Examination

March / April – 2011

Electronics : Paper - IV

(Digital Electronics & Microprocessor)

Time : Hours]

[Total Marks : 70

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
 Fillup strictly the details of signs on your answer book.

Name of the Examination :
 S. Y. B. Sc.

Name of the Subject :
 Electronics - 4

Subject Code No. : 0 7 1 6 Section No. (1, 2,.....) : Nil

Seat No. :

Student's Signature

- (2) Q.1 is compulsory .
- (3) Figures at extreme right indicate full marks.
- (4) Abbreviations have their usual meanings.

- 1 Answer in brief. 14
- (a) Define parity bit.
 - (b) Distinguish between synchronous and asynchronous counter.
 - (c) Distinguish between combinational circuit and sequential circuit.
 - (d) What do you understand by level, positive, and negative triggering of flip-flop ?
 - (e) Convert 24568_{10} and 8567_{10} to binary number.
 - (f) Encode 1101011101_2 to even parity Hamming Code.
 - (g) What do you understand by Flag register in 8085 A microprocessor ?

- 2 (a) Simplify the following expression using Boolean Laws. 5+5+4

$$(A + B) \left(A + \bar{B} \right) \left(\bar{A} + B \right) \text{ and } \bar{X} (X + Z) + \bar{A} + AZ$$

- (b) Add each of the following in 9's and 10's complement.
 $-489_{10} + 375_{10}$ and $(-549_{10}) + (-235_{10})$

- (c) Add the following in 1's and 2's complement.
 $-452_{10} + 228_{10}$ and $372_{10} + 129_{10}$

OR

- 2 (a) Using K-map simplifies the following and implements it using appropriate hardware **5+5+4**

$$E = \sum m (0, 1, 2, 4, 6, 8, 9, 11, 14) + d(13,15)$$

$$F = \pi M (0, 2, 3, 5, 7, 8, 10, 12, 14) + d(1, 9,15)$$

- (b) Draw the digital circuit diagram of the following expression.

$$\overline{A}\overline{B} + C(D + \overline{E}) + AD + (\overline{A}E + D\overline{E}).B$$

$$CDE + A(\overline{C} + E) + BC + A(C + DE)$$

- (C) Convert the following into its equivalent Gray code.
 1110010110111_2 and 101110110101011_2

- 3 (a) Draw the circuit diagram for the RS Flip-flop **7+5+2** and explain its working. Extend your discussion for the Clocked RS Flip-flop.
(b) Explain the working of the D Flip-flop.
(c) State the drawback of the RS Flip-flop.

OR

- 3 (a) Write a program in 8085 A for finding smallest **5+5+4** number from among the five numbers stored at appropriate consecutive memory locations.
(b) Write a program in 8085 A for finding the sum of the five numbers stored at appropriate consecutive memory locations. Program should take care of the possible 16-bit resultant sum.
(c) State the importance of the 'stack' and 'stack register'.
- 4 (a) Draw the 3-bit ripple counter and explain its working **5+6+3** with help of clock diagram.
(b) Draw the decade counter and explain its working with help of clock diagram.
(c) Define modulo counter.

OR

- 4 (a) Explain the function of the state diagram with **5+5+4** suitable example.
(b) Explain the operation of shift register.
(c) Define 'State diagram' and 'state table'.

- 5 (a) State the application of XOR and XNOR gates. **6+4+4**
(b) Prove that NAND and NOR as universal logic gates.
(c) Design and implement half and full adder circuit.

OR

- 5 (a) Draw and explain, in detail the architecture of **5+5+4**
8085 A microprocessor.
(b) Explain, in detail, the flag register of 8085 A
microprocessor.
(c) Explain the following instruction of 8085 A
microprocessor.
ANI data , SBI data , CMP M , DAD D.