

## Sample Question Paper – I

9037

Course Name :- Computer Engineering Group  
Course code :- CO/CM/CD/IF  
Semester :- Third  
Subject :- Digital Techniques  
Duration :- 3 hours

Marks: 80

**Instructions:**

1. All questions are compulsory.
2. Figures to the right indicates full marks.
3. Use of non-programmable calculator is permissible.

**Q 1: Attempt any Eight of the following:** (8 x 2 = 16)

- a) Define Fan-out & Noise margin.
- b) Represent timing diagram of digital signal for positive & negative logic in TTL.
- c) Compare TTL & CMOS logic families(any four points).
- d) Draw logic symbol & truth-table for EX-OR gate.
- e) Simplify using Boolean algebra-

$$A.B + \bar{A}.B + \bar{A}.\bar{B}$$

- f) Draw block diagram of 4:1 MUX and give its truth table.
- g) Draw Full Adder using two Half adders.
- h) Draw neat diagram of clocked S-R flip-flop & write its truth-table.
- i) Differentiate between static & dynamic RAM
- j) Give the classification of different types of semiconductor memories.

**Q 2: Attempt any Three of the following:** (4 x 3 = 12)

- a) Draw circuit for i) AND using NOR ii) OR using NAND.
- b) State & prove De Morgan's Theorems.
- c) Prove using De Morgan's Theorem –

$$\text{i) } (A + B) + (C + D) = \overline{\overline{(A + B)} \cdot \overline{(C + D)}}$$

$$\text{ii) } A.B + C.D = \overline{\overline{A.B} \cdot \overline{C.D}}$$

- d) Realize the following Boolean expression using basic gates.

i)  $Y = \overline{(A + C)} (B + C)$

ii)  $Y = \overline{A}.B + B.\overline{C}$

**Q 3: Attempt any Three of the following:**

**(4 x 3 = 12)**

- a) Draw 9-bit odd parity generator using IC 74180.
- b) Draw & explain half subtractor.
- c) Implement the following function using 8:1 MUX.

$$Y = \sum m(0, 2, 3, 6).$$

- d) Implement following expression using NAND gates only.

$$Y = A.B + \overline{B}.C + C.\overline{A}$$

**Q 4: Attempt any Four of the following:**

**(4 x 4 = 16)**

- a) Describe the function of 4-bit SISO shift register with the help of block diagram, truth-table, timing diagram.
- b) State four applications of counters.
- c) What is race around condition? How it can be avoided?
- d) Compare RAM & ROM.
- e) Design Asynchronous MOD-10 Counter.
- f) Draw neat diagram of R/2R ladder type DAC. Find its output expression.

**Q 5: Attempt any Three of the following:**


**(4 x 3 = 12)**

- a) List advantages & disadvantages of Ramp type ADC.
- b) Draw block diagram of Digital Comparator IC 7485 & write its function table.
- c) Describe four specifications of DAC.
- d) An 8-bit converter is driven by 500 KHz clock. Find –
  - i) Maximum conversion time
  - ii) Average conversion time.

**Q 6: Attempt any Three of the following:**

**(4 x 3 = 12)**

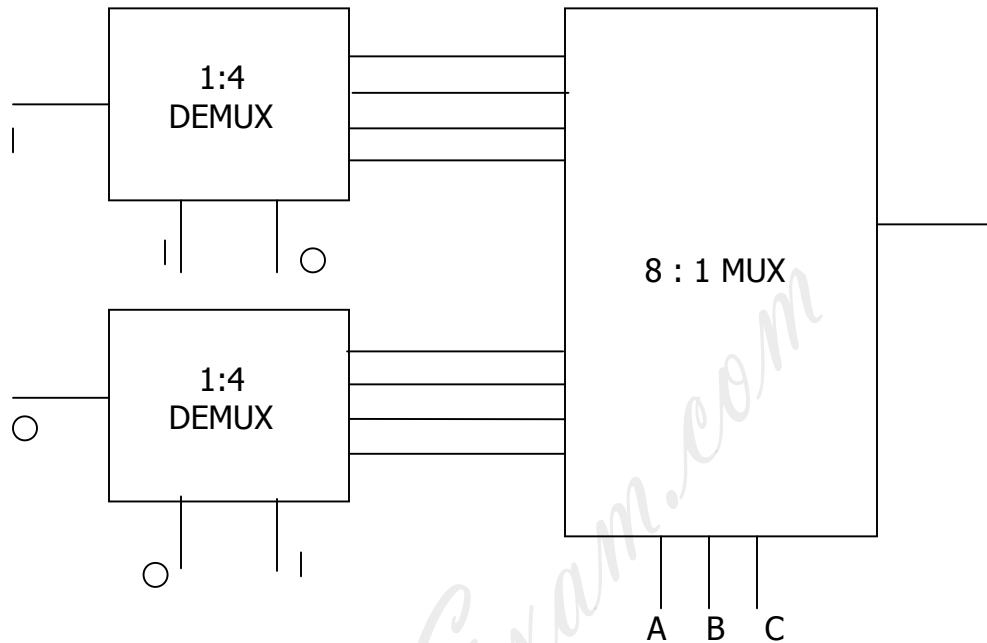a) Determine 8:1 MUX output as select inputs A,B,C change from 000 to 111.



- b) Describe edge triggering & level triggering with respect to flip-flop.
- c) An 8 MHz square wave clocks a 5-bit ripple counter. What will be the frequency at output of last flip-flop & the duty cycle of this counter.
- d) Differentiate Synchronous & Asynchronous Counter (any four points).