

Sample Question Paper – I

9042

Course Name :- **Electronics & Video Engineering**
Course code :- **EV**
Semester :- **Third**
Subject :- **Electronic Circuit and Application**
Duration :- **3 hours**

Marks: 80

Instructions :

- 1] All questions are compulsory.
- 2] Figures to the right indicates full marks.
- 3] Use of non-programmable calculator is permissible.

Q 1: - Attempt any Eight

16 Marks

- a) Draw a symbol of 1) Photodiode 2) Phototransistor.
- b) Draw characteristic of UJT.
- c) List the specification of MOSFET.
- d) What is the necessity of tuned circuit?
- e) State Barkhausen criteria.
- f) What is the necessity of wave shaping circuit?
- g) Define Bandwidth
- h) Define 1) line regulation 2)load regulation.
- i) How Schmitt trigger is different from multivibrator?
- j) List the IC's used for voltage-regulated power supply.

Q 2: - Attempt any Three

12 Marks

- a) Explain working principle of UJT
- b) Draw constructional diagram of n-channel and p-channel JFET.
- c) What are the advantages of negative feed back?
- d) Draw and explain RC phase shift oscillator.

Q 3: - Attempt any Three

12 Marks

- a) Draw neat circuit. diagram of transistorized colpitt oscillator and give formula for output frequency.
- b) What is stagger tuning? How it employed in the tuned voltage amplifier.
- c) What are the application of RC integrator (any four)
- d) With neat sketch explain the working of astable multivibrator.

Q 4: - Attempt any Two

16 Marks

- a) What are the types of FET biasing circuit? Explain any one in detail.
- b) Draw and explain transistorized series voltage regulator.
- c) What are the types of current time base generator? Explain in detail bootstrap Generator.

Q 5: - Attempt any Three


12 Marks

- a) Draw circuit diagram of single tuned amplifier by showing I/p and o/p waveform
- b) What are the types of nonlinear circuit?
- c) How transistor acts as switch? Explain with neat sketch.
- d) Draw and explain Schmitt trigger circuit with I/p o/p waveform.

Q 6: - Attempt any three

12 Marks

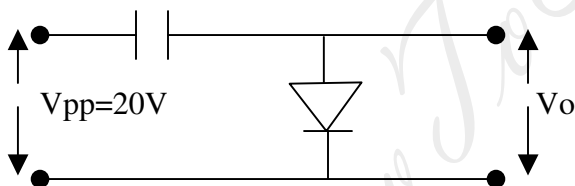- a) Compare series and parallel resonance circuit. w.r.t. following point.
 - 1) Frequency response
 - 2) impedance at resonance
 - 3) Bandwidth
 - 4) current at resonance
- b) Identify the circuit. and also draw I/p and o/p waveform of following circuit.



- c) Illustrate the troubleshooting approach in astable multivibrator.
- d) Describe wave shaping and also explain why it is needed in practical application?