

Sample Question Paper-I

Course Name : Industrial Electronics

9074

Course Code : IE

Semester : IV

Title of the Subject : Power Electronic

Max Marks : 80

Time : 3Hrs.

Instructions:

1. All questions are compulsory.
2. Illustrate your answers with neat sketches wherever necessary.
3. Figures to the right indicate full marks.
4. Assume suitable data if necessary.
5. Preferably, write the answers in sequential orders.

Q.1. A) Attempt any four.

08 Marks

- 1) Draw & label the symbols of
 - 1) GTO 2) SUS 3) SCS 4) LASCR
- 2) Draw the circuit of UJT oscillator triggering SCR.
- 3) What is forced commutation? List methods of forced commutation.
- 4) Draw the circuit of Class B commutation of SCR.
- 5) Draw ideal characteristics of switch. What is the on state voltage of ideal switch.


Q.1. B) Attempt any two .

08 Marks

- a) i) Define the terms with respect to SCR
 1. Holding current
 2. Latching current
- ii) Given SCR is in ON state, if anode current is reduced continuously, state at what current SCR turns off.
- b) Study the circuit diagram and answer the following.
 1. Identity the circuit

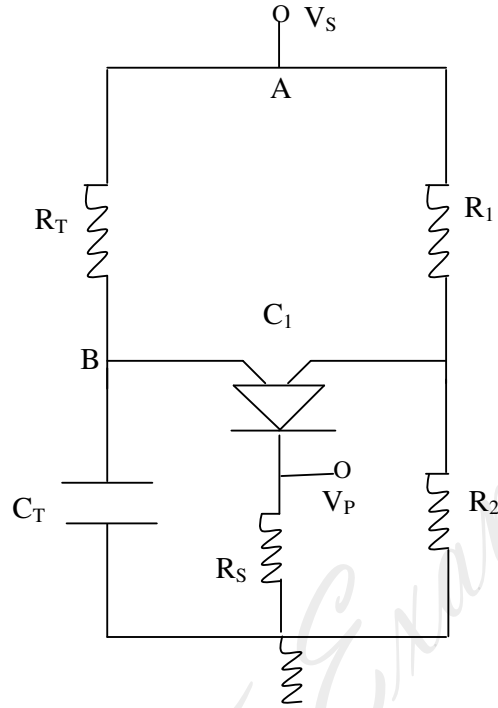2. State the expression for output frequency.
3. Find the of frequency of output.

$$R_T = 1k\Omega, C_T = 0.1 \mu f, R_1 = 24 k\Omega, R_2 = 12k\Omega$$



- c) State the four modes of operation of Triac. Which are the efficient modes and why?

Q.2. Attempt any three.

12 Marks


- a) Draw transistorized equivalent circuit of SCR. State its operation.
- b) Why Diac is used to trigger triac? Draw the relevant circuit diagram.
- c) Why the triggering mechanism $V_{AK} > V_{BO}$ is not used in controlled rectifier.
- d) State the meaning of finger voltage of SCR. In parallel combination of two SCRs , State the effect of difference in finger voltage on operation of SCRs

Q.3. Attempt any three.

12 Marks

- a) Draw circuit of symmetrical half controlled 1ϕ bridge rectifier. Draw wave forms of
 1. Input voltage
 2. Firing pulse
 3. Load current
 4. Load voltage
- b) Draw power flip flop using SCR. State its working
- c) With what modification the given circuit will work as one of the standard commutation. Explain the operation of modified circuit.

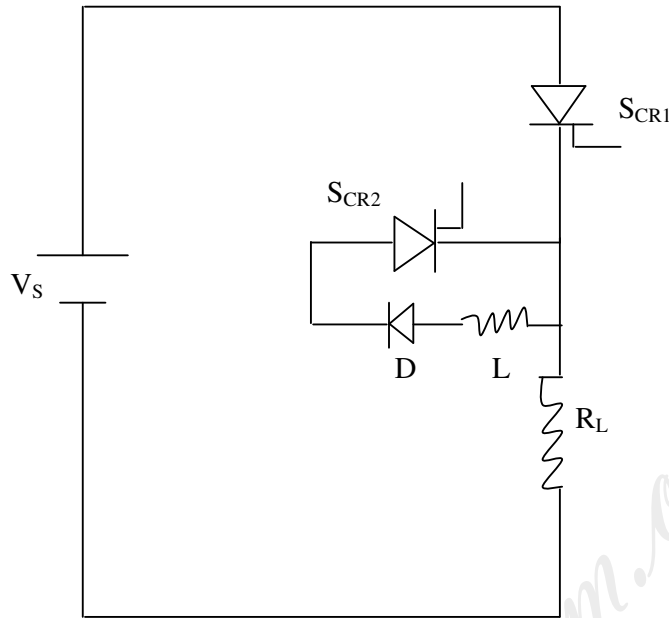
d) Draw circuit of Triac as static ac switch. What are the merits of triac static switch over SCR static switch.



Q.4. Attempt any two.

16 Marks

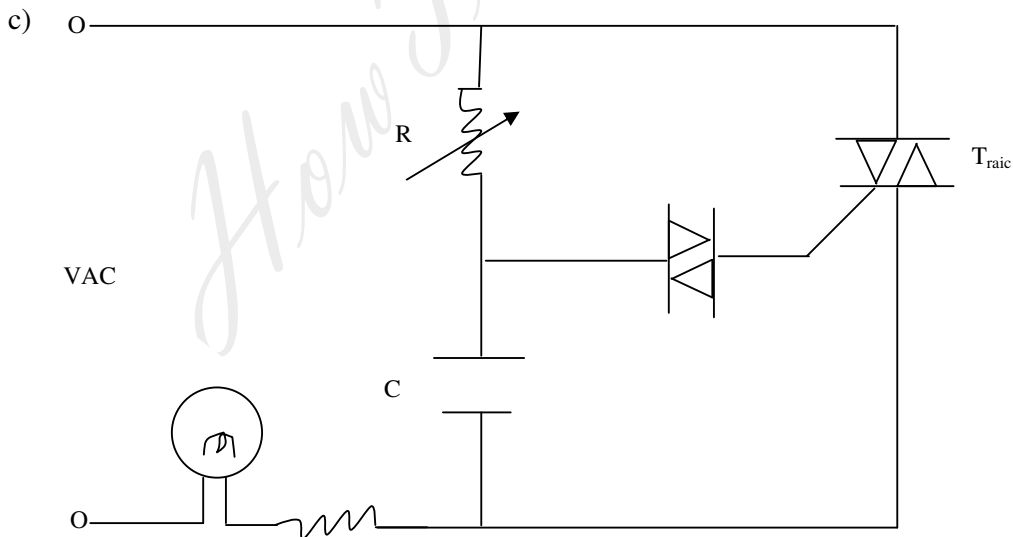- a) Draw circuit of flasher using SCRs. State its working. State one application of it.
- b) Draw circuit of 3 ϕ controlled half wave rectifier. State the meanings and condition for continuous conduction and discontinuous conduction operation. Draw the corresponding wave forms



- 1) Identify the circuit.
- 2) What is the effect of increase in R on load Justify.
- 3) Modify the circuit to control speed of ac motor.


Q.5. Attempt any three.

12 Marks

- a) Define with respect to GTO.
 - 1. Maximum controllable anode current.
 - 2. Maximum gate to cathode reverse voltage.
- b) In a circuit the operating current is 800 A and operating voltage is 1000 V. The available SCRs are with maximum current rating 200 A and voltage rating 500V. Using available SCRs how above circuit can be developed?
- c) What will happen if anode current is more than rated value of maximum controllable anode current? Why PUT is called programmable UJT? How it is programmed.
- d) Draw circuit of single phase controlled bridge rectifier with inductive load. Stated its working.

Q.6. Attempt any three.

12 Marks

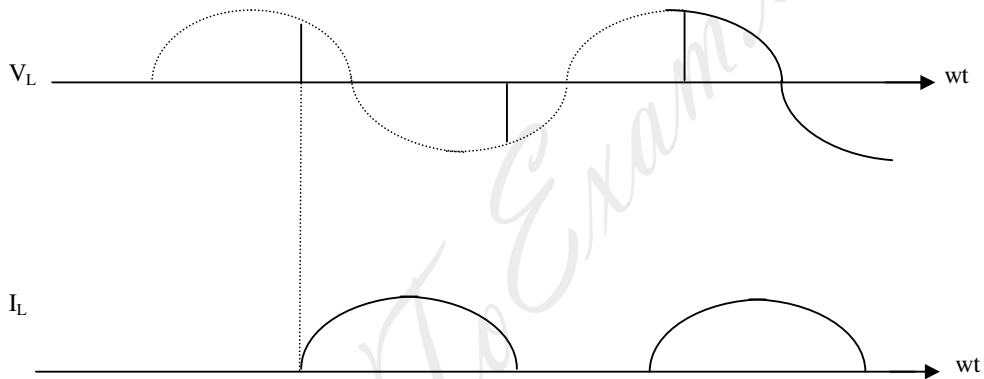

- a) It is desired to obtain the above I_L & V_L wave forms suggest the appropriate rectifier circuit with load. Draw the circuit and state type of the quadrant operation
- b) What are the conditions for commutation of SCR?
- c) Draw circuit of Mc Murray Bed ford commutation method to commutate SCR. State its operating principle
- .d) How dc output voltage is controlled in single phase half wave rectifier. Give expression for dc output voltage & rms output voltage.