

MANIPAL INSTITUTE OF TECHNOLOGY, MANIPAL
(A Constituent Institute of Manipal University, Manipal)

THIRD SEMESTER B.E. DEGREE MAKEUP EXAMINATION
(REVISED CREDIT SYSTEM)

22 July 2009

ANALOG ELECTRONIC CIRCUITS (ELE 209)

Time: 3 hours

Max. Marks: 50

Note : Answer any **FIVE** full questions.
Missing data, if any, may be suitably assumed.

- 1A. Determine I_D , V_0 for the circuit shown in *Figure Q1A*, given $V_D=0.7V$. (02)
- 1B. Draw the output voltage for the circuit shown in *Figure Q1B*. (06)
- 1C. Write a technical note on construction and applications of photo diode. (02)

- 2A. Plot the waveform of V_0 for the circuit shown in *Figure Q2A*. (02)
- 2B. Design a voltage divider bias circuit to meet the following specifications. $V_{CC}=24V$, $V_{CE}=4.5V$, $I_C=10mA$, $\beta_{dc}=100$, $S(I_{CO})\leq 5$, $R_E=280\Omega$. (04)
- 2C. Derive the expression of stability factor $S(I_{CO})$ and $S(V_{BE})$ for collector-base feedback bias circuit. (04)

- 3A. Draw the low frequency small signal h-parameter model for the circuit shown in *figure Q3A*. Also identify the configuration employed in the circuits for both transistors. (02)
- 3B. For the circuit shown determine A_v , A_{vs} , R_o and R_i . Given $h_{ie}=1.1K$, $h_{re}=2.5\times 10^{-4}$, $h_f=50$, $h_o=24\mu A/V$. (04)
- 3C. Derive expression for calculating the voltage gain A_v , current gain A_i , input impedance Z_i and output admittance Y_o of an amplifier using hybrid parameters. (04)

- 4A. Discuss the effect of cascading of amplifiers on bandwidth and gain. (02)
- 4B. For the network shown in *Figure Q4B*, find V_G , I_{DQ} , V_{GSQ} , V_D , V_S and V_{DSQ} . Given $I_{DSS}=10mA$, $V_P=-4V$. (04)
- 4C. For the CE amplifier shown in *Figure Q4C*, determine the bandwidth if $h_{ie}=1.2K$, $h_{fe}=100$, $r_0=\infty$. (04)

- 5A. Write a brief note on distortion in power amplifiers (02)
- 5B. For a transformer coupled class-A power amplifier, derive an expression for efficiency and hence obtain maximum efficiency. Also list advantages and disadvantages of the same. (04)
- 5C. A series fed class A amplifier has $R_B=2K$, $R_C=20\Omega$, $\beta=25$ and $V_{CC}=25V$. Draw the circuit and determine DC input power, efficiency, and power dissipated. Assume the peak value of base current due to AC input voltage is 10Ma. (04)

- 6A. Determine the output power and Zener diode current for the circuit shown in *Figure Q6A*. Given $\beta=75$. (02)
- 6B. Explain the working of a transformer based series voltage regulator. (04)
- 6C. Design a LM317 based variable voltage regulator for 5 to 15V range supplying not more than 100mA load current. (04)

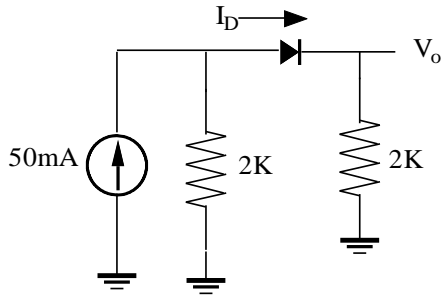


figure Q1A

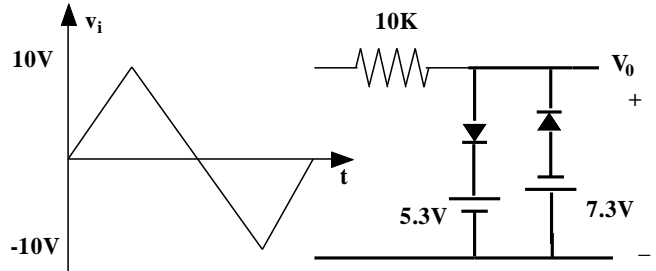


Figure Q1B

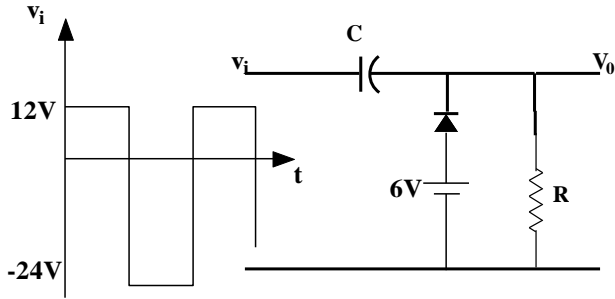


figure Q2A

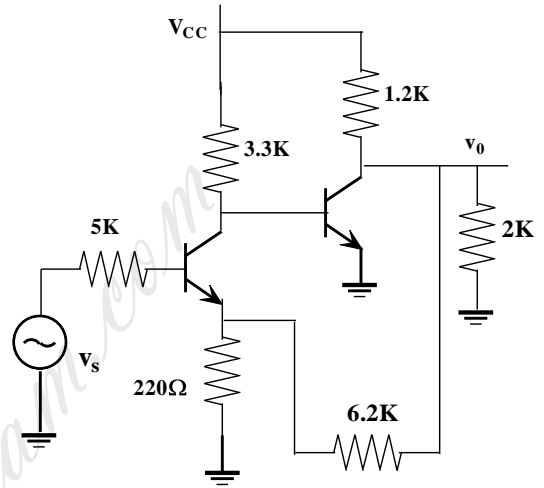


figure Q3A

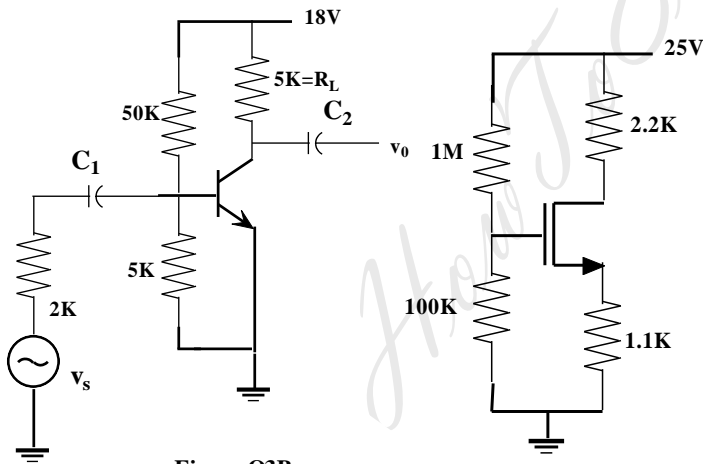


Figure Q3B

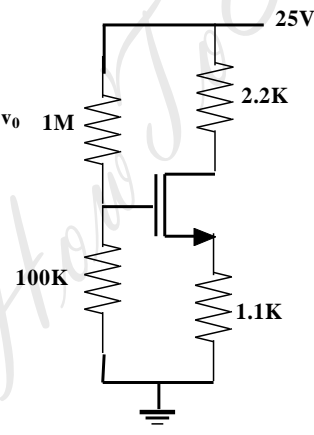


figure Q4B

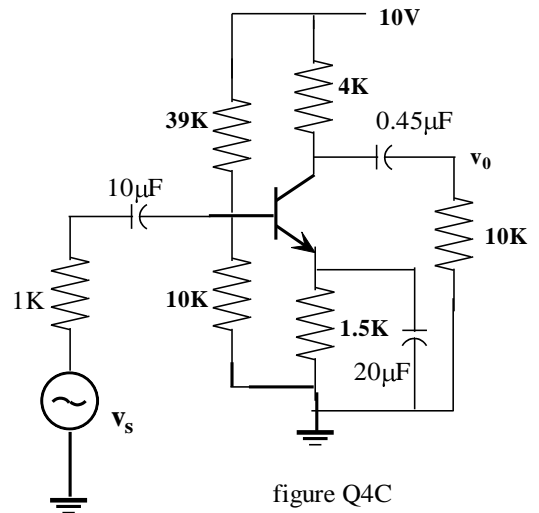


figure Q4C

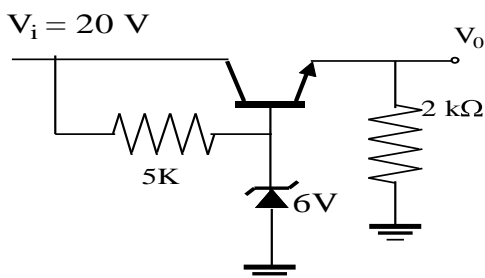


figure Q6A