



MANIPAL INSTITUTE OF TECHNOLOGY

(A Constituent Institute of Manipal University)

Manipal – 576 104



THIRD SEMESTER B.E. DEGREE SUMMER/ MAKE UP EXAMINATIONS JULY 2008

SUBJECT: ELECTRONIC DEVICES & CIRCUITS (BME 201)

(REVISED CREDIT SYSTEM)

Monday, July 28, 2008: 2.00 - 5.00 p.m

TIME: 3 HOURS

MAX. MARKS: 100

Instructions to Candidates:

1. Answer any FIVE full questions.
2. Draw labeled diagram wherever necessary

1. (a) With V-I Characteristics explain the operation of a pn diode. Write the current equation. Also find the diode current if a forward bias of 0.7 Volt is applied to a silicon diode having a maximum reverse saturation current of 100 nano ampere. 08
- (b) Explain the operation of a SCR with its V-I characteristics and mention its applications. 07
- (c) Explain the operation of a photo diode with its characteristics. Mention its applications. 05
2. (a) Draw a common emitter npn transistor circuit. Draw its input and output characteristics and explain all the operating regions. Also derive the relation of collector current in active region. 10
- (b) Draw a neat diagram of n-channel enhancement type MOSFET and explain its operation with drain and transfer characteristics. 10
3. (a) Draw the circuit of a UJT and draw its V-I characteristics and explain. Also give a application of UJT and explain. 10
- (b) Explain the various steps observed in the fabrication of Integrated Circuits. List its advantages. 10
4. (a) Draw the circuit of a common source FET amplifier with source resistance. Draw its small signal model and derive the relation of the voltage gain. 10

- (b) For the circuit shown in fig.Q4b, assume $h_{FE} = 100$, (i) Find if the silicon transistor is in cutoff, saturation or in active region and find V_o . 10
(ii) find minimum value of emitter resistor R_E for which the transistor operates in the active region.
5. (a) Derive the relations of the stability factors S and S^1 of a self biased transistor circuit. 08
(b) Write a note on zener diode 06
(c) Write a note on bias compensation in transistor circuits. 06
6. (a) Draw a single stage CE transistor amplifier circuit. Draw its h-parameter model. Derive the relations of various gains, input and out impedances. 10
(b) Draw a hybrid- π model of a transistor in the CE configuration and discuss on the circuit components. 10

Figures