

Reg. No.										
----------	--	--	--	--	--	--	--	--	--	--



**MANIPAL INSTITUTE OF TECHNOLOGY**  
 (A Constituent Institute of MAHE – Deemed University)  
 Manipal – 576 104



**THIRD SEMESTER B.E. DEGREE MAKE-UP EXAMINATIONS January 2007**

**SUBJECT: NETWORK ANALYSIS (BME 203)**  
 (REVISED CREDIT SYSTEM)

Tuesday, January 09, 2007: 9.00 a.m.- 12.00 noon

**TIME: 3 HOURS**

**MAX. MARKS: 100**

**Instructions to Candidates:**

1. Answer any FIVE full questions.
2. Draw labeled diagram wherever necessary

- |    |  |    |
|----|--|----|
| 1. | (A) Find the equivalent resistance between XY in the network of Fig 1.A  | 08 |
|    | (B) For the network shown in Fig 1.B show that the equivalent network is replaced by $V_{\theta} = (V_1/2)(1+a+b-ab)$ and $Z_{\theta} = (3-b)/2$ .   | 08 |
|    | (C) Explain the concept of Maximum Power Transfer Theorem.   | 04 |
| 2. | (A) For the network of Fig 2.A find $Z_L$ for maximum power at the load and determine the maximum power.   | 08 |
|    | (B) For the network shown in Fig 2.B write the mesh current equations. Find the power output of the voltage source and determine the power in the circuit resistors.   | 08 |
|    | (C) Write note on : i) Driving point impedance ii) Nodal analysis  | 04 |
| 3. | (A) In the network shown in Fig 3.A switch K is changed from position a to b at $t=0$ . Solve for $i$ , $di/dt$ , $d^2i/dt^2$ at $t=0^+$ .   | 08 |
|    | (B) Establish a relation between: i) Impedance of the Series tuned circuit with quality factor ii) Bandwidth of a series tuned circuit with quality factor.  | 06 |
|    | (C) For the circuit of Fig 3.C find the value of $R_1$ such that the circuit is at resonance.  | 06 |
| 4. | (A) A series RLC circuit has a resistance of $10\Omega$ , a capacitance of $100\mu F$ and a variable inductance. The applied voltage is $230V, 50Hz$ . Find i) the value of inductance for which the voltage across the resistance is maximum. ii) Quality factor iii) Voltage drops across R, L, and C. | 08 |
|    | (B) Explain the following terms: i) Selectivity ii) Quality factor iii) Bandwidth  | 06 |
|    | (C) The network of Fig 4.C is in steady state with the switch K closed. At $t=0$ switch is opened. Find $V_K$ at $t=0^+$ and $dV_K/dt$ at $t=0^+$ .  | 06 |
| 5. | (A) Find the laplace transform of the waveforms given in Fig 5.A.  | 10 |
|    | (B) Express i) Z parameters in terms of Y parameters ii) ABCD parameters in terms of Y parameters.   | 10 |
| 6. | (A) For the circuit shown in fig 6.A, Find the drop across $R_L$ .   | 10 |

- (B) i) Find the inverse laplace of the following: a)  $5/s(s^2+16)$  b)  $(s+5)/s(s^2+6s+9)$  05
- ii) Show that a)  $L\{t f(t)\} = -\frac{d}{ds} F(s)$  b)  $L\{f(t)/t\} = \int F(s) ds$  05

*HowToExam.com*

*HowToExam.com*

