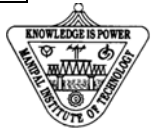


Reg. No.										
----------	--	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY
Manipal University, Manipal – 576 104
FIRST SEMESTER B.E. DEGREE END SEMESTER EXAMINATION
December –2007
SUBJECT: BASIC ELECTRONICS (ECE – 101/102)
(REVISED CREDIT SYSTEM)



TIME : 3 HOURS

MAX. MARKS : 50

Instructions to candidates

- Answer ANY FIVE full questions.
- Missing data may be suitably assumed.

- 1A. List the characteristics of ideal OPAMP. 3
- 1B. Simplify the following Boolean expression and realize using NAND gates
- $$F = (A + B + C)(A + B + C)(A + B)$$
- 3
- 1C. What is amplitude modulation? Derive equation for AM output in time domain. Sketch sinusoidally modulated AM wave for modulation index $m = 1$, $m < 1$ and $m > 1$. 4
- 2A. Explain AND gate with help of a circuit using discrete components. 3
- 2B. Explain the need for modulation. 3
- 2C. Assume that a silicon transistor with $\beta = 80$, $V_{CC} = 16V$, $R_C = 3.9 K$, $R_E = 0.68K$, $R_1 = 62K$ and $R_2 = 9.1K$ is used in voltage divider bias circuit. Determine the operating point. 4
- 3A. With the help of energy band diagrams classify solids. 3
- 3B. Define α and β . Derive the relationship between them 3
- 3C. Primary voltage to a transformer with turns ratio is 5:1 is 120V, 60Hz. This is applied to bridge rectifier employing 4 identical diodes with forward voltage drops 0.6V and forward resistance 15Ω . The load resistance is $1k\Omega$. Calculate average and rms load voltage, efficiency, ripple factor, PIV rating and frequency of output waveform. 4
- 4A. What is doping ? Compare P and N type semiconductors. 3
- 4B. Explain half adder with functional table and write logical expressions for sum and carry. Realize carry using NOR gates. 3

- 4C. i) For the zener regulator $V_i = 16\text{ V}$, $R_S = 1\text{ K}$, $V_Z = 10\text{ V}$ and $R_L = 3\text{ K}$. Determine V_o , I_Z and P_Z
ii) Repeat with $R_L = 1\text{ K}$ 4
- 5A. Perform the following
(i) $(257.75)_{10} - (128.825)_{10}$ using binary 2's complement arithmetic
(ii) $(ABCD)_{16} = (?)_{10} = (?)_2 = (?)_8$ 3
- 5B. Sketch the frequency response of RC coupled amplifier and mark the regions and indicate bandwidth 3
- 5C. A silicon diode has reverse sat current 12 nA at 20°C . (a) Find the diode current when it is forward biased by 0.65 V . Find the diode current when the temperature rises to 100°C . 4
- 6A. For a differential amplifier, the input voltages are $v_1 = 10\text{ mV}$ and $v_2 = 8\text{ mV}$. If the differential gain is 5000 , Calculate the output voltage when the CMRR is 80 dB . 3
- 6B. Draw the circuit diagram of OPAMP adder and derive the expression for output. 3
- 6C. With help of circuit diagram and waveforms explain working of center tapped full wave rectifier. 4
