

(b) Implement the following logic functions :

(i)  $X = \bar{A} + BC$  using NAND gates only

(ii)  $Y = \bar{A}B + C$  using NOR gates only

5

7. (a) Write the truth table of half-adder and full-adder. Draw their logic diagrams. 4

(b) Convert the following Boolean expression into equivalent SOP form. 3

$$ABC + \bar{A}\bar{B} + ABC\bar{C}$$

(c) Distinguish between multiplexer and demultiplexer. Draw the logic diagram of 4-to-1 line multiplexer. 3

8. Answer the following questions (any two):

5+5

(a) Explain the temperature effects on the V-I characteristics of a diode.

(b) Derive expressions of output voltages for both inverting and non-inverting amplifier.

(c) Describe with examples the standard forms of Boolean expressions.

(d) Describe the Ideal and Real characteristics of op-amp.



Total number of printed pages – 7

B. Tech

BE2101/BENG 1105

Second Semester Examination – 2009

**BASIC ELECTRONICS**

Full Marks – 70


Time : 3 Hours

*Answer Question No. 1 which is compulsory and any five from the rest.*

*The figures in the right-hand margin indicate marks.*

1. Answer the following questions : 2×10
- (a) Explain with suitable examples the difference between analog, digital and discrete-time signals.
  - (b) Compare the advantages and disadvantages between centre-tapped and bridge-type full -wave rectifier.

P.T.O.

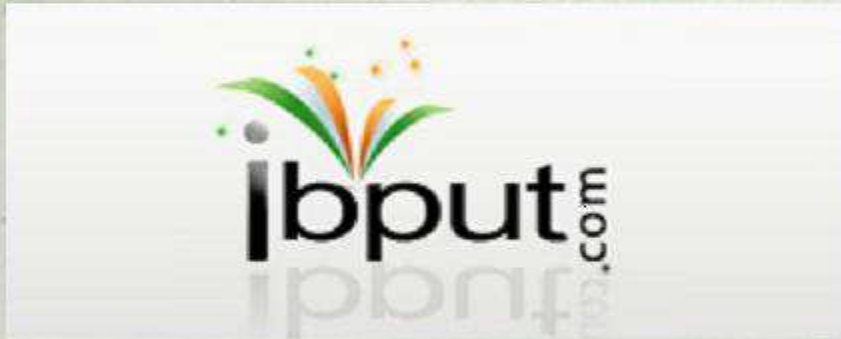


*How To Exam*

- (c) Define the following terms :
  - (i) Slew rate of an op-amp
  - (ii) Unity gain bandwidth
- (d) Derive the expression for the collector current for a CE Transistor.
- (e) Distinguish between ac and dc load line.
- (f) Explain with suitable diagrams the difference between self-bias and fixed-bias.
- (g) Determine the number of cycles of 1 KHz sinusoidal signal as viewed on an oscilloscope when the sweep frequencies are
  - (a) 2 KHz and
  - (b) 500 Hz.
- (h) Binary number system is used in digital electronics circuits. Why octal, decimal or hexadecimal number systems are not used in circuit levels ?
- (i) Convert the decimal number - 39 to its equivalent 1's complement and 2's complement forms.

- (j) Compare static - RAM and dynamic-RAM with respect to their speed, volume of data storage, size and cost.


2. (a) What is a clamper circuit ? Draw the circuit diagram of a positive clamper and a negative clamper showing their output waveforms. 5

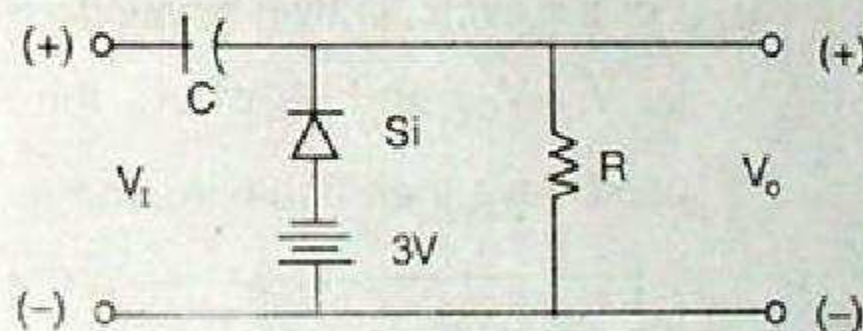(b) Analyze and draw the output waveform of the following circuit when  $V_i = 5 \sin(100\pi t)$ . 5




3. (a) Define mobility of charge carrier. Which of these following materials (Si, Ge and GaAs) will have the best thermal stability? Why ? 3

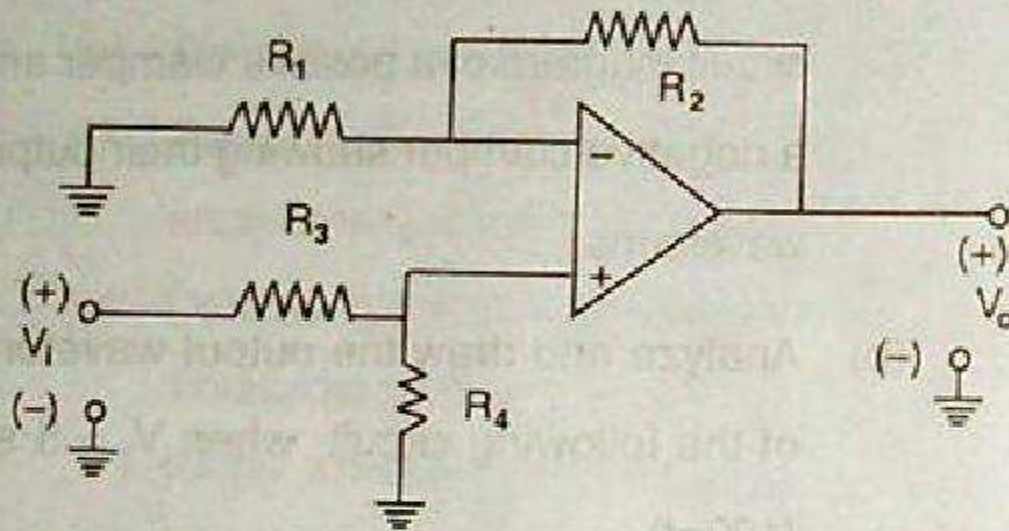- (b) Distinguish between zener breakdown and Avalanche breakdown. 2
- (c) Derive an expression for the voltage gain of the given op-amp circuit. 5



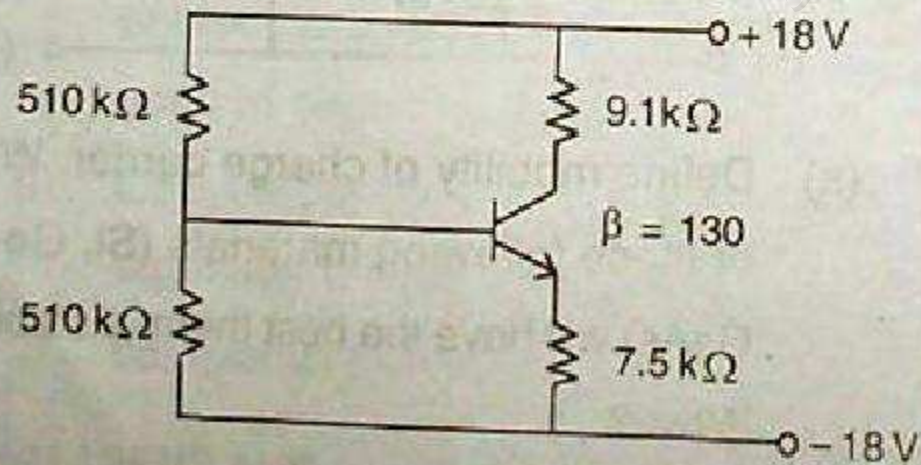4. (a) For the circuit shown below determine  $I_B$ ,  $I_C$ ,  $V_E$ ,  $V_{CE}$  and  $V_B$  where the symbols used have their usual meaning. 5



- (b) Draw a simplified hybrid model of CE transistor amplifier and then find its input impedance, output impedance and voltage gain. 5

5. (a) Explain the basic principle of sinusoidal oscillator. How does an oscillator start its operation? What is its voltage gain during starting and during its normal operation? 5

- (b) State and explain the function of the sweep signal in an oscilloscope. What is Lissajous method? Does Lissajous method require sweep signal? Justify answers in brief along with suitable diagram or graphs. 5

6. (a) Which logical gates are considered as Universal gates? Draw the circuit diagrams showing the universal properties of any one Universal gate. 5

