

Total number of printed pages – 7 **B. Tech**
CPES 5201

Fourth Semester Examination – 2008

NETWORK THEORY

Full Marks – 70

Time : 3 Hours

*Answer Question No. 1 which is compulsory
and any **five** from the rest.*

*The figures in the right-hand margin
indicate marks.*



1. Answer the following questions : 2×10
- (i) Give at least three properties of parallel resonance circuit.
 - (ii) What are half power frequency points ? Explain.

- (iii) What is the difference between an ideal filter and a practical filter ?
- (iv) Give the properties of a filter.
- (v) What are even and odd functions ? Give examples.
- (vi) What is the nature of the impulse response of an RL circuit ?
- (vii) For the band pass filter what is the normal characteristic impedance ?
- (viii) What is the value of ramp function at $t=0$?
- (ix) What is the reciprocal of a driving point function ?
- (x) State final value theorem.

P.T.O.

CPES 5201

2


Contd.

2. (a) Define the following network functions with reference to a 2-port network : 4

(i) driving point impedance

(ii) transfer impedance.

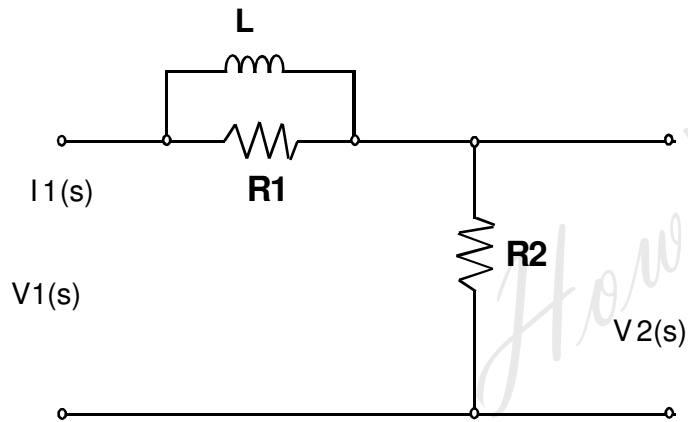(b) For the given network, find the transfer functions $G_{21}(s)$, $Z_{21}(s)$ and driving point impedance $Z_{11}(s)$. 6



3. (a) What do you understand by : 4

(i) zeros of a function, and

(ii) zeros of transmission.

(b) What information do poles and zeros provide in respect of a network to which they relate ? Draw pole and zeros for : 6

$$\frac{s^2 + 3s + 2}{s^2 + 7s + 12}$$

And evaluate $v(t)$ either analytically or by making use of pole-zero diagram.

4. (a) Derive the expression of Z-parameters in terms of other parameters. 5

(b) Calculate the Z-parameters, if the values of other parameters are given below : 5

(i) $A = 2, B = -1, C = 3$ and $D = -2$

(ii) $h_{11} = 1, h_{12} = -2, h_{21} = -3, h_{22} = 2$

(iii) $Y_{11} = 1/3, Y_{12} = 2/3, Y_{21} = -1/3, Y_{22} = 1/6$

5. (a) Draw and discuss the profile of circuit parameters with frequency in a parallel resonant circuit. 3
- (b) Derive the relationship between Bandwidth, Detuning Factor, Quality factor, Impedance and selectivity of a parallel resonant circuit. 3
- (c) A current source, having an internal resistance of $10\text{ K}\Omega$ feeds a tank circuit containing a coil (having $L_C = 200\text{ mH}$, $R_C = 10\ \Omega$) in parallel to a capacitor of $100\ \mu\text{F}$. Find the frequency of resonance and Q factor. 4
6. (a) Discuss the basic concept of working of low pass and high pass filters using reactive elements. 3

CPES 5201

5

P.T.O.

- (b) Analyze a prototype High Pass Filter. 3
- (c) Design the T and π section of a prototype High Pass Filter having cut-off frequency of 20 kHz and design impedance of $450\ \Omega$ s. Also find its characteristics impedance and phase constant at 25 kHz as well as determine the attenuation at 4 kHz . 4
7. (a) Represents the given impedance function using Cauer-I form. 5

$$Z(s) = \frac{s^2 + 1}{s^2 + 2}$$

- (b) Synthesize the Foster-II form of given admittance function 5


$$Y(s) = \frac{s^2 + 1}{s^2 + 3}$$

CPES 5201

6

Contd.

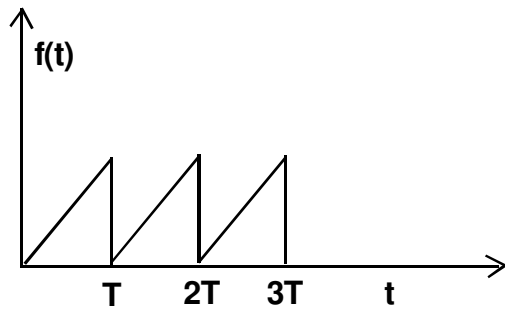8. (a) Determine the effective value of $f(t)$ of the waveform shown in the figure below. 5



- (b) Obtain the Fourier coefficients for the function given by 5
 $f(t) = (t + \pi)$ when $-\pi < t < \pi$; $f(x+2\pi) = f(x)$

HowToExam.com