

5. (a) A soft iron ring of relative permeability of 2000 has a mean diameter of 75 cm and a cross sectional area of 20 cm². A radial airgap of 2 mm width is cut in the ring that is wound with a coil of 1500 turns. Calculate the current required to produce an airgap flux of 0.55 milli-weber. Neglect leakage and fringing. Given $\mu_0 = 4\pi \times 10^{-7}$ H/m. 5

(b) A single-phase two winding transformer is designed to operate at 230/115 V, 50 Hz. Calculate the magnitude of the secondary no-load voltage and its frequency if the high voltage side of the transformer is connected to 2+2+1

- (i) 230 V, 40 Hz
- (ii) 115 V, 25 Hz
- (iii) 230 V dc

6. (a) A coil is connected in series with a capacitor of 10 micro-farads and the series combination is connected across a 250 V single-phase ac mains. The resistance of the coil is 3.5 ohms. What

must be the inductance of the coil in order that maximum current occurs at a frequency of 5


- (i) 30 Hz
- (ii) 40 Hz
- (iii) 110 Hz ?

(b) A balanced three phase star connected load of 250 kW takes a lagging current of 200 A with a line voltage of 1000 V, 50 Hz. Find the circuit constants (resistance and inductance) of the load per phase. 5

a) Derive the mathematical expression for the charge stored in the capacitor of a R-C series circuit connected across a d.c voltage source. 4

b) The emf (electromotive force) per turn for a single phase, 2200/220 V, 50 Hz transformer is approximately 15 volts. Calculate

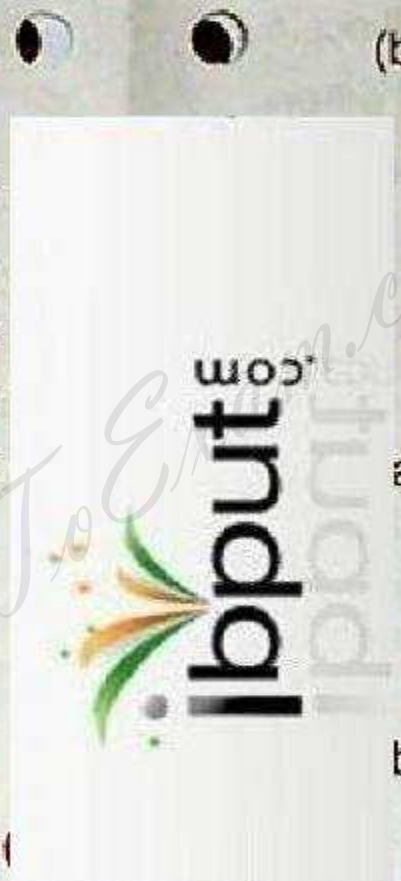- (i) the number of primary and secondary turns and



- (ii) the net cross sectional area of the core, for a maximum flux density of 1.25 Wb/m^2 in the core. 3+3

8. (a) Explain with the help of a block diagram the principle of power generation in a nuclear power plant. 5

(b) A moving coil instrument gives a full scale deflection of 25 mA when potential difference across its terminals is 250 mV . Calculate 5

- (i) the shunt resistance for measuring currents up to 25 A and
(ii) series resistance for measuring voltage up to 500 V .



Second Semester Examination – 2009

BASIC ELECTRICAL ENGINEERING

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any five from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10
- (a) Three resistance of 12 ohms , 24 ohms and 30 ohms magnitude are connected in series and the series combination is connected across a 220 volts d.c. source. Compute the power dissipated in each resistor and the total power drawn from the source.

- (b) Four resistance of 15 ohms, 30 ohms, 35 ohms and 50 ohms magnitude are connected in parallel across a 230 volts d.c. source. Compute the power dissipated in each resistor and the total power drawn from the source. What is the total current ?
- (c) An inductor of inductance 50 milli-henries is connected in series with a capacitance of 10 micro-farads. Find the impedance of the circuit when the frequency is
- (i) 50 Hz and
 - (ii) 5 kHz
- (d) A direct voltage of 200 V is applied to a coil of resistance 20 ohms and inductance of 2000 milli-henries. Find the time taken for the current through the coil to reach one-half of its final value.
- (e) A resistor of 25 ohms in series with a 0.45 micro-farad capacitor is connected across a supply at 270 V, 70 Hz. Find the current through the capacitor.

- (f) A Circuit consists of a resistor of 10 ohms in series with an ideal inductor of 4.5 henries. The frequency is 70 Hz. Calculate the conductance and the susceptance of the circuit.
- (g) A 3-phase balanced star-connected load is connected to a symmetrical 3-phase 440 V balanced supply. The current in each phase is 60 amperes and lags 45 degrees behind the corresponding phase voltage. Find the phase voltage and the total power.
- (h) An iron ring with a circular cross section of 7.5 cm diameter and a mean circumference of 150 cm is wound with a coil of 750 turns. Calculate the flux in the magnetic circuit for an exciting current of 2.5 A in the coil. The relative permeability of iron is 1600 and μ_0 equals $4\pi \times 10^{-7}$ H/m.
- (i) What do you mean by the term 'slip' of a three-phase induction motor ? Calculate the 'slip' of a six-pole induction motor



running at 960 RPM while drawing power from a 50 Hz three-phase balanced source.

(j) Two admittances $0.025 \angle -50^\circ$ and $0.015 \angle 45^\circ$ are connected in parallel. Find out the resultant impedance in rectangular form.

2. (a) Using Superposition Theorem, find the current flowing in the 40-ohm resistor in Fig.1 below. 6

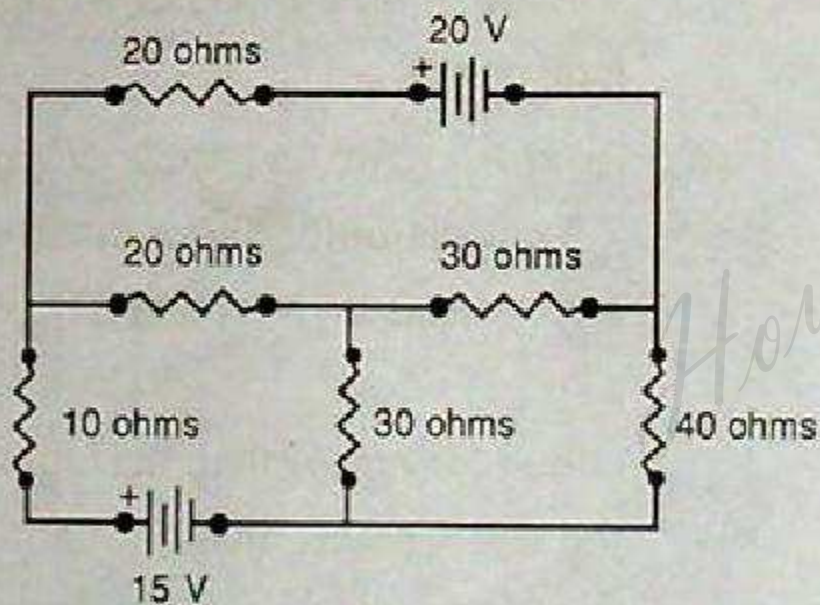


Fig - 1

(b) State and briefly explain 'Thevenin's Theorem' with one example. 4

3. (a) Describe the voltage build up process in a d.c. shunt generator. Define 'critical field resistance'. 5

(b) A single-phase a.c. supply voltage of 230 V at 50 Hz is applied to a coil of inductance 4.5 henries and resistance of 2.25 ohms in series with a capacitance C. Calculate the value of the capacitance C so as to obtain a potential difference of 255 V across the coil. 5

(a) A 3-phase, 3-wire, 415 volts, 50 Hz, RYB system of balance supply is connected to a delta connected load with $Z_{RY} = 120 \angle 40^\circ$ ohms, $Z_{YB} = 155 \angle 50^\circ$ ohms and $Z_{BR} = 100 \angle -30^\circ$ ohms. Obtain the three line currents and draw the complete phasor diagram showing the line voltages, line currents and phase currents. The supply neutral is earthed. 7

(b) What are the expressions for
(i) the 'torque developed' and
(ii) 'back emf induced' in a d.c. shunt motor?

Explain all the terms in the expressions very briefly. 3