

B.Tech. Degree IV Semester Examination, April 2009

EB/EC/EI/EE 406 INDUSTRIAL AND POWER ELECTRONICS (2006 Scheme)

Time: 3 Hours

Maximum Marks: 100

PART – A

(Answer all questions)

(8 x 5 = 40)

- I
- a) Explain the turn-off mechanism of an SCR.
 - b) Draw and explain half wave RC trigger circuit for an SCR.
 - c) Explain the difference between a half controlled bridge and fully controlled bridge.
 - d) Explain the function of a freewheeling diode, showing how it is connected in the circuit.
 - e) Explain auxiliary commutation scheme for SCR.
 - f) Explain various PWM techniques used in inverters.
 - g) Explain with circuit, $\frac{dv}{dt}$ protection for thyristors.
 - h) What is dielectric heating? Write applications

PART – B

(4 x 15 = 60)

- II Draw the V.I characteristics of a TRIAC and explain its working in each of the four modes using appropriate diagrams. (15)
- OR
- III a) What are the various methods to turn-on an SCR. (7)
b) Explain the working principle of thyristars using two-transistor analogy. Also device necessary equations. (8)
- IV Draw and explain the various voltage wave forms of a single phase full wave controlled rectifier (with discontinuous load current) with the armature of a d.c. Motor as load. (15)
- OR
- V Draw the circuit of a three phase full wave rectifier with R load and explain its working. With suitable waveforms. (15)
- VI a) Explain the working of Jones Chopper. (10)
b) Explain the working of single-phase series inverter. (5)
- OR
- VII a) Briefly explain the concept of slip power recovery scheme in the speed control of Induction Motors. (10)
b) Describe the principle of d.c. Chopper operation. (5)
- VIII a) Explain online and off line UPS with the help of block diagram. (8)
b) A Boost regulator has an input voltage of $v_{in} = 15V$. The average output voltage is $v_{av} = 25V$ and average load current $I_{av} = 0.5A$. If $L = 150 \mu H$ and $C = 200 \mu F$ determine
i) Duty cycle
ii) Ripple current in inductor
iii) Ripple voltage of filter capacitor
Assume the switching frequency as 25 KHz. (7)
- OR
- IX a) What is induction heating? Explain its principle. Briefly explain any two applications of induction heating. (10)
b) What is a static switch? List the merits of static switches over mechanical switches. (5)

