http://www.howtoexam.com

Set No. 1

IV B.Tech I Semester Supplimentary Examinations, May/Jun 2009 ELECTRONIC MEASUREMENTS AND INSTRUMENTATION (Electronics & Communication Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks ****

- 1. (a) Explain with a neat block diagram of a dual slope digital voltmeter.
 - (b) A dual slope integrating type of A/D converter has an integrating capacitor of 0.1 microfarad and a resistance of 100k.ohms connected. If the reference voltage is 2V, and the output of an integrator is not to exceed 10V, what is the maximum time reference voltage. [6+10]
- 2. (a) With respect to construction and circuit configuration, explain how a square wave generator differs from sine wave generator.
 - (b) With a neat block diagram discuss about an AF sine wave generator. [8+8]
- 3. (a) Draw and discuss the spectral displays of various modulations using Spectrum analyzer.
 - (b) Explain one application of distortion factor meter. [8+8]
- 4. (a) What are the advantages of dual beam for multiple trace oscilloscopes?
 - (b) How is the vertical axis of an oscilloscope deflected? How does this differ from horizontal axis? [8+8]
- 5. (a) When is period measurement preferred over frequency measurement? Also give two conditions for the period measurement.
 - (b) With a suitable block diagram, explain the operation of a pre scaled frequency counter. [8+8]
- 6. (a) With neat sketch explain the measurement of unknown inductance by using Hay's bridge? What are the advantages and limitations of it.
 - (b) What are the limitations of wheat stone bridge? [12+4]
- 7. (a) Compare RTD with thermistor.
 - (b) Explain how the displacement is measured using LVDT. [8+8]
- 8. (a) Explain how an electrical transducer can be used to find the unknown pressure of a liquid?
 - (b) Briefly explain the principle and operation of piezoelectric accelerometer?[8+8]

http://www.howtoexam.com

Set No. 2

IV B.Tech I Semester Supplimentary Examinations, May/Jun 2009 ELECTRONIC MEASUREMENTS AND INSTRUMENTATION (Electronics & Communication Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks ****

- 1. (a) Draw the block diagram of the measuring system and explain the function of each stage of this system.
 - (b) Explain the types of test signals used in determining dynamic characteristics of measurements applied to a system. [8+8]
- 2. (a) What are the precautionary measures to be taken in a signal generator application?
 - (b) Discuss in detail about RF signal generators operation. [8+8]
- 3. (a) Distinguish between spectrum analyzer and harmonic distortion analyzer.
 - (b) Explain the operation of a wave analyzer with a neat diagram. [8+8]
- 4. (a) Draw the neat diagrams of both vertical and horizontal deflection systems and explain briefly about their working.
 - (b) Draw the block diagram of a dual beam oscilloscope and explain its working. [10+6]
- 5. (a) Explain the operation of 10 to 1 probe.
 - (b) Explain the operation of the spot wheel method for frequency measurement. $[8{+}8]$
- 6. Define Quality factor? Derive the expression of Quality factor in Hay's bridge which is used for the measurement of unknown inductance? [16]
- 7. (a) With neat sketch, explain the resistance pressure transducers in detail?
 - (b) Derive an expression for poissons ratio. [8+8]
- 8. (a) Explain how an electrical transducer can be used to find the unknown pressure of a liquid?
 - (b) Briefly explain the principle and operation of piezoelectric accelerometer?[8+8]

http://www.howtoexam.com

Set No. 3

IV B.Tech I Semester Supplimentary Examinations, May/Jun 2009 ELECTRONIC MEASUREMENTS AND INSTRUMENTATION (Electronics & Communication Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks ****

- 1. (a) What is Ayrton Shunt? Describe it with a neat sketch. Specify its applications.
 - (b) Design a universal Ayrton shunt to provide an ammeter with a current range of 2A, 5A, 10A using a d'Arsonval movement with an internal resistance $R_m = 50\Omega$ and full scale deflection current of 1mA. [6+10]
- 2. (a) With a neat diagram describe the principle of operation of Random pattern generator.
 - (b) Explain with a block diagram the working of a AF signal generator. [8+8]
- 3. (a) Explain how distortion occurs during transmission of a waveform or communication signal.
 - (b) Explain about various types of distortions occurring in signals. How can they be analyzed [8+8]
- 4. (a) With a neat block diagram, describe the working of a triggered sweep CRO.
 - (b) Mention the advantages of general purpose oscilloscope. [10+6]
- 5. (a) Explain the operation of 10 to 1 probe.
 - (b) Explain the operation of the spot wheel method for frequency measurement. [8+8]
- 6. (a) With neat sketch explain how unknown resistance measured by means of wheat stone bridge?
 - (b) What are the applications of wheat stone bridge? And list out its limitations. [8+8]
- 7. (a) Describe the operation of Optical pyrometers.
 - (b) Explain the working of a turbine flowmeter with a neat diagram. [8+8]
- 8. (a) Explain briefly the construction and working of the Hydraulic Force Meter and also explain its applications in various measurements?
 - (b) Find the cause that produces the resistance or obstruction to a 10kg body, moving with an acceleration of 10kg/m^2 . Name the cause and find the value of that cause? [8+8]

Set No. 4

IV B.Tech I Semester Supplimentary Examinations, May/Jun 2009 ELECTRONIC MEASUREMENTS AND INSTRUMENTATION (Electronics & Communication Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions All Questions carry equal marks ****

- 1. (a) Explain the functioning of a potentiometer type digital voltmeter.
 - (b) A $3\frac{1}{2}$ digit of DVM has an accuracy of ± 0.5 percent of reading ± 1 digit.
 - i. What is the possible error in volt, when the instrument is reading 5.00 V on the 10 V range?
 - ii. What is the possible error in volt, when reading 0.1 V on the 10 V range? [8+8]
- 2. (a) What is the need for inserting isolation between the signal generator output and oscillator in a simple signal generator? What are the different ways in which this can be achieved?
 - (b) With the help of a block diagram, explain the working of laboratory type pulse generator. [8+8]
- 3. (a) Draw and discuss the spectral displays of various modulations using Spectrum analyzer.
 - (b) Explain one application of distortion factor meter. [8+8]
- 4. (a) With a neat block diagram, explain the function of each block of a general purpose oscilloscope.
 - (b) Mention the advantages of general purpose oscilloscope. [10+6]
- 5. (a) With a suitable block diagram and waveforms, explain the operation of a frequency counter.
 - (b) How many displays (total decades) should a frequency counter have if its accuracy and resolution are to be 0.001 percent? [10+6]
- 6. (a) Explain the "parallel-connection" method of using Q-meter and Obtain the expressions for resistance, reactance and Q factor.
 - (b) Give the list of the detectors used in ac bridges. [10+6]
- 7. (a) What parameters should be considered in selecting a transducer?
 - (b) Define active transducer and passive transducer? Give the examples for each? [8+8]
- 8. (a) With a neat sketch, briefly explain the principle of operation and force measurement by cantilever beam type load cell?

Set No. 4

(b) Explain the working of D.C. Tachogenerators with a neat sketch. What are its advantages and limitations? [8+8]

How