

Code No. A5402

NR

JAWAHARLAL NEHRU TECHNOLOGY UNIVERSITY, HYDERABAD

M.Tech. I Semester Regular Examinations, March – 2009

ANALYSIS OF POWER ELECTRONIC CONVERTERS

(Common to Power Electronics & Electric Drives, Power Electronics,
Electrical Power Engineering and Power Engineering & Energy Systems)

Time: 3 hours

Max. Marks.60

Answer any Five questions
All questions carry equal marks

- 1.a) Explain about synchronous tap changers. Give the applications.
- b) The single-phase full wave controller supplies an RL load. The input rms voltage is $V_s = 120$ V, 60 Hz. The load is $L = 6.5$ mH and $R = 2.5$ Ω . The delay angles of thyristors are equal $\alpha_1 = \alpha_2 = \pi/2$. Determine:
 - i) The conduction angle of thyristor T_1 Si
 - ii) The rms thyristor current I_R
 - iii) The input power factor.
- 2.a) The three phase unidirectional controller supplies a Y-connected resistive load with $R = 2.5$ Ω and the line-to-line input voltage is 208 V (rms), 60 Hz. If the desired output power is $P_0 = 12$ KW. Calculate:
 - a) the delay angle, α
 - b) the rms output phase voltage V_0 , and
 - c) the input PF
- b) What are the advantages and disadvantages of ac voltage controllers?
- 3.a) What is a cyclo converter? Explain the principle and operation of single-phase cyclo converter with neat diagram draw the waveforms.
- b) What are the effects of load inductance on the performance of cyclo converters?
- 4.a) What is pulse-width modulation control of converts and what are the applications?
- b) A single phase full converter is connected to RLE load. The source voltage is 230 V, 50 Hz. The average load current of 10 A is continuous over the working range. For $R = 0.4$ Ω and $L = 2$ mH, compute firing angle delay for $E = 120$ V.
5. For a 3 phase full converter, sketch the input voltage waveforms for V_{ab} , V_{ac} , V_{bc} etc and voltage variation across any one thyristor for one complete cycle for a firing angle delay of:
 - a) 60° and
 - b) 120°

Contd...2

Code No. A5402

::2::

- 6.a) How can the input current of the rectifier-fed boost converter be made sinusoidal and in phase with the input voltage?
- b) The buck regulator has an input voltage $V_s=15$ V. The required average out put voltage $V_a=5$ V and the peak-to-peak out put ripple voltage is 10 mV. The switching frequency is 20 KHz. The peak-to-peak ripple current of inductor is limited to 0.5A. Determine:
- the duty cycle K,
 - the critical values of L and C.
7. Explain the voltage control of single phase inverters with the help of waveforms.
- 8.a) What are the techniques for harmonic reductions?
- b) Explain about the back and boost inverter and give the advantages and applications.

HowToExam.com