

34

Roll No.

Total No. of Pages : 3

BT-4/J07

8764

Digital Electronics

Paper-ECE-204 E

Time : Three Hours]

[Maximum Marks : 100

Note :- Attempt FIVE questions in all, selecting at least ONE question from each part. Each question carries equal marks.

PART-I

1. Perform the indicated operation :-

- (i) Determine the decimal value of $(0.325)_{10}$.
- (ii) Discuss the self complementing property of excess-3 code.
- (iii) Add the following BCD numbers :-
 $01100111 + 01010011$
- (iv) Convert $(2469)_{10}$ to BCD.
- (v) Subtract $94_{10} - 5C_{16}$.
- (vi) Convert $F80B_{16}$ to Binary.
- (vii) Divide 01100100 by 00011001 using sign magnitude arithmetic.
- (viii) Subtract the following binary numbers (Signed Number) :-
 $00001100 - 11110111$.
- (ix) Find 2's complement of 10111000 .
- (x) Multiply the binary numbers: 101×111 . 10×2=20

2. (a) Using Q-M algorithm find a minimal cover for the following function :-

$$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 7, 8, 10) + d(3, 11, 15).$$

15

(b) Draw the circuit and discuss their characteristic tables for the following gates :-

(i) OR gate using NAND gates only.

(ii) EX-OR and EX-NOR gates using NOR gates only. 5

PART-II

3. (a) A combinational circuit is defined by the following three functions :-

$$F_1 = \bar{X} + Y, F_2 = XY + \bar{X}\bar{Y}$$

$$F_3 = \bar{X}\bar{Y} + XYZ$$


Design the circuit with a decoder and external gates. 10

(b) Draw a logic diagram of 2-line to 4-line decoder / demultiplexer using NOR gates only. 5

(c) Design a 3-Bit Binary to Gray Code Converter. 5

4. (a) Draw a 4-Bit parallel-in serial-out shift register. Draw the timing diagram for outputs. 10

 (h) For the state diagram shown below, design the circuit using 'D' FFs.



10

PART-III

5. (a) What is basic difference in saturated and non saturated logic families? Describe the operation of a basic ECL and prove that the transistors in ECL are never driven to saturation region. 10

(b) What are the limitations of DTL over TTL? 5

(c) Modify 'DTL' circuit to use in high noise environment. 5

- (a) What is Interfacing ? Discuss the interfacing between CMOS and TTL. 10
- (b) Discuss the advantages and disadvantages of CMOS over TTL. 5
- (c) Explain the operation of a CMOS NOR gate. 5

PART-IV

- (a) Write a short note on each of the following :-
 - (i) Weighted Resistor DAC
 - (ii) Dual Slope ADC. 10
- (b) Explain the specifications for ADC and DAC which must be satisfied. 10
- (a) Design a BCD to Excess -3 Code converter using a
 - (i) PROM (ii) PLA (iii) PAL. 15
- (b) Discuss the architecture for a PLD. Give some suitable examples. 5

HowToExam.com