

FACULTY OF ENGINEERING

B.E. II/IV Year (ECE) II Semester (Main) Examination, April/May 2008

(New)

NETWORKS AND TRANSMISSION LINES

Time : 3 Hours]

[Max. Marks : 75

Answer **all** questions of Part A.


Answer **five** questions from Part B.

Smith charts can be used.

Part A – (Marks : 25)

1. Derive the condition for reciprocity in terms of ABCD parameters. 3

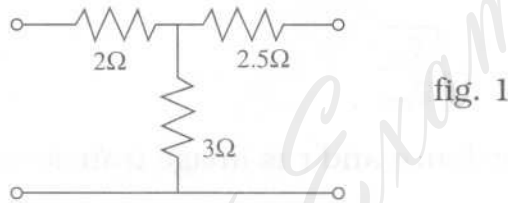2. Find  $\pi$  network for T network shown in fig. 1. 3




3. Show the two two port networks connected in series and in cascade. 2

4. Define insertion loss for the two port network. 2

5.  $25\Omega$  line is terminated by  $100\Omega$  load. What will be VSWR and reflection coefficient on the line? 3

6. Sketch the input reactance of a short circuited line for  $0 < l < \lambda$  as a function of  $\beta l$ . 3

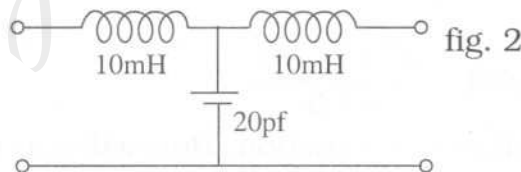7. Find the  $Z_0$  for filter section shown in fig. 2. 3



8. By sketching the reactance of series and shunt arms as a function of frequency, find the filter type and cut off frequency for fig. 2. 2

9. What do you understand by loading of line? What is the purpose of loading? 2

10. Explain the use of short and open stubs. 2

[P.T.O.

**Part B** – (Marks : 5 × 10 = 50)

11. Find the  $\gamma$  parameters of network in fig. 3.

10

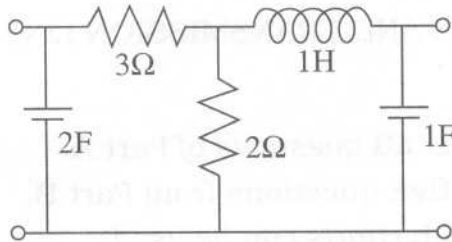


fig. 3

12. (a) Show that ABCD matrices multiply to find overall ABCD matrix when networks are connected in cascade.

5

(b) Design symmetrical T attenuator for  $R_o = 600\Omega$  and attenuation of 20dB.

5

13. (a) For a two port network show that .

$$Z_0 = \sqrt{Z_{sc}Z_{oc}} \text{ and } \text{Tan hr} = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

Where  $Z_0$  is charac. impedance and r is image transfer constant.

6

(b) For network of fig 4 find expression for  $\cos h r$  where r is  $\alpha + j\beta$ .

4

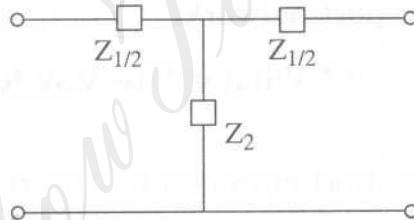


fig. 4

14. Design composite filter for  $R_o = 600\Omega$ ,  $f_c = 1000\text{kHz}$  and  $f_\infty = 1200\text{kHz}$ . Filter should have low pass T sections. Sketch approx. attenuation characteristics for each section.

10

15. (a) Synthesize the function  $Z(s) = \frac{s^2 + 2s + 6}{s + 3}$ .

5

(b) List the properties of positive real function. How will you test Hurwitz polynomial?

5

16. (a) Show that for open circuited line of length l, propagation const.  $\beta$  and charac. impedance  $Z_o$  the input impedance is  $Z_{oc} = jZ_o \cot \beta l$ . Sketch this function as a function of frequency.

7

(b) Find the length and charac. impedance of quarter wave transformer to match 500 line to 2000 load at 1GHz

3

17. Write short notes on (any **two**) :

10

- (a) Smith chart and its applications
- (b) Distortion in transmission lines.
- (c) Equalizers.