

FACULTY OF ENGINEERING

B.E. II/IV Year (ECE) II Semester (Main) Examination, April/May 2008

(New)

ANALOG ELECTRONIC CIRCUITS

Time : 3 Hours]


[Max. Marks : 75

Answer **all** questions of Part A.

Answer **five** questions from Part B.

Part A – (Marks : 25)

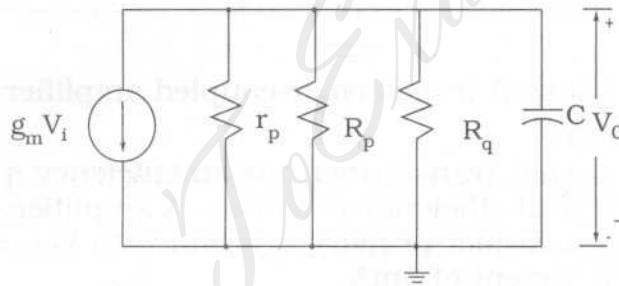1. Draw the output wave of a Class AB amplifier.
2. Calculate the mid band gain $A_o \equiv V_o/V_i$ for this circuit.



(for $R_p \ll r_p$ and $R_p \ll R_g$)

3. Draw the complementary symmetry amplifier circuit.
4. Why Class AB mode is preferred?
5. Define a Dominant pole.
6. What happens to R_{of} , R_{if} in current series feed back circuit?
7. Briefly explain unilaterisation.
8. Define selectivity.
9. Explain the function of a catcher/free-wheeling diode.
10. How EMI is reduced in switching regulators?

Part B – (Marks : 5 × 10 = 50)

11. Give an approximate expression relating f_H^* and the 3-dB frequencies of n-nonidentical stages. For two and three identical stages, What is f_H^* / f_H . 10
12. The parameters of the transistors in the circuit shown in Fig.1 are $h_{fe} = 50$, $h_{ie} = 1100\Omega$ and $h_{re} = h_{oe} = 0$. Find (a) the mid band gain (b) the value of C_b necessary to give a lower 3-dB frequency of 20Hz. (c) Find the value of C_b necessary to ensure less than 10% tilt for a 100Hz square-wave input. 10

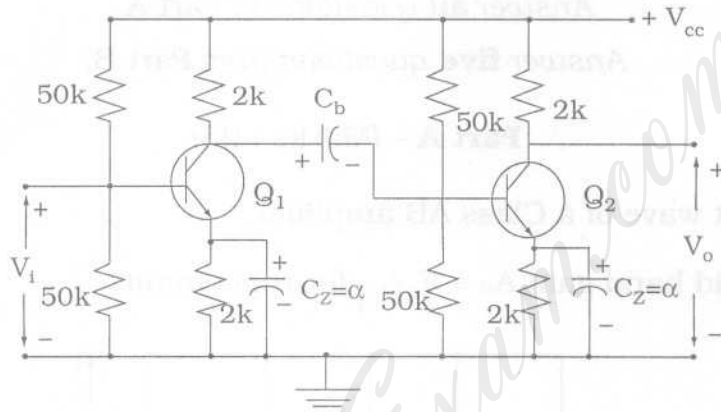


Fig. 1

13. (a) Draw a complete Class-A transformer-coupled amplifier and derive its theoretical efficiency. 10
 (b) Assume that the output transformer has an efficiency $\eta = 80\%$. Calculate the maximum practical efficiency in Class – A amplifier, if the power delivered to the transformer primary is 20mn with $V_{cc} = +13V$ and the Collector quiescent current of 5mA. 10
14. Explain the principle and operation of a Class – D amplifier with the help of a block diagram. 10
15. For two transistors in cascade with feed back from the second emitter to the first base through the resistor R' . If the block capacitors and biasing resistors are neglected, derive the expression for A_{vf} . 10
16. (a) Draw the circuit diagram of a RC-phase shift oscillator, using IC Op amplifier and mention the frequency of oscillation and condition of oscillation. 5
 (b) Explain the principle and operation of the Colpitt's oscillator using FET as an amplifier. 4
 (c) Why RF-chokes are used in LC-oscillators. 1
17. (a) Draw a transistorized double tuned amplifier and its equivalent circuit. 4
 (b) Design a single tuned amplifier to operate a centre frequency of 455 kHz, a BW of 10 kHz with the given parameters for the transistor $g_m = 0.04 A/V$, $h_{fe} = 100$, $C_{b'e} = 1000 PF$, $C_{b'c} = 10 PF$, $Q = 100$. The bias network and Input resistance are adjusted so that $R_i = 5k\Omega$ and $R_L = 500 \Omega$. 6