

Code No.: 10046

**FACULTY OF ENGINEERING**

**B.E. II/IV Year (ECE) II Semester (Main) Examination, April 2006**

**ANALOG ELECTRONIC CIRCUITS**

Time : 3 Hours]

[Max. Marks : 75

Answer **all** questions of Part A.

Answer **five** questions from Part B.

Assume any data if missing.

**Part A – (Marks : 25)**

1. Sketch the frequency response of a transformer coupled amplifiers. Give the reasons for the fall in gain at low and high frequencies. 3
2. What is the range of frequency in terms of ' $f_T$ ' upto which the hybrid- $\pi$  equivalent circuit of CE amplifier is valid? 2
3. What is harmonic distortion in power amplifiers and why does it occur? 2
4. Why class AB is preferred over class B in audio frequency power amplifiers. 2
5. An amplifier has an open loop voltage gain  $1000 \pm 100$ . If 10% negative feedback is introduced, what will be its closed loop voltage gain and its variation? 3
6. Comment why RC oscillators cannot be used at radio frequencies. 2
7. What factors decide the frequency stability of an oscillator? 3
8. Sketch the frequency response of a staggered tuned amplifier. State its advantages over cascaded single tuned amplifiers. 3
9. State the advantages of class C power amplifiers over class B tuned power amplifiers. 2
10. What are the limitations of zener voltage regulators and how do you over-come them? 3

[P.T.O.

**Part B - (Marks : 5 × 10 = 50)**

- 1. (a) Explain the role of emitter bypass capacitance on the low frequency response of an RC coupled CE amplifier. 4
- (b) A BJT is tuned to have  $f_T = 500$  MHz,  $g_m = 100$  mmhos,  $h_{fe} = 100$  and  $C_{bc} = 5$  pF. It is used as an CE amplifier with  $R_s = 1$  K $\Omega$  and  $R_L = 2$  K $\Omega$ . Assume  $r_{bb'} = 0$ . Determine for the amplifier (i) the mid-band voltage gain ( $v_o/v_s$ ) and (ii) upper 3-dB cutoff frequency. 6
- 2. (a) What is cross over distortion in class B push pull amplifier and how do you eliminate it? Explain your answer with a neat circuit diagram and waveforms. 4
- (b) A power transistor is used as a class A transformer coupled amplifier and is to deliver a maximum of 5 watts to a 4 ohm load. Operating point is adjusted for symmetrical clipping with collector supply voltage of 20V. Assume ideal characteristics with  $V_{min} = 0$ . Calculate for the amplifier (i) Transformer turns ratio (ii) peak collector current and (iii) collector circuit efficiency. 6
- 3. (a) Prove that negative feedback in amplifiers reduces the distortion. State the assumptions made in your derivation. 4
- (b) Design a colpitts oscillator to oscillate at 1 MHz using a BJT having  $h_{ie} = 2$  K $\Omega$  and  $h_{fe} = 100$ . Use capacitances of 1000 pF and 500 pF. Show the circuit diagram with all the component values along with biasing circuit. Derive the expressions used in your design. 6
- 4. (a) What is the possibility of oscillations in a tuned amplifier? How do you neutralize a BJT tuned amplifier against oscillations. Explain your answer with a neat circuit diagram and derive the expressions for the neutralizing components. 5
- (b) Draw the circuit diagram of a double tuned transformer coupled voltage amplifier using a BJT. Derive the expressions for its voltage gain at the centre frequency and band-width for critical coupling. 5
- 5. (a) State the advantages of SMPS over conventional voltage regulator. Show the block schematic diagram of a SMPS and explain its operation. 5
- (b) An unregulated D.C. source of  $(12 \pm 2)$  V is available and is to be regulated using a zener diode to provide 6 V at 25 mA. A 6 V zener diode is available. Show the circuit diagram with the component values. What is its output impedance? 5

6. (a) A BJT has  $h_{ie} = 2 \text{ K}\Omega$ ,  $h_{re} = 10^{-5}$ ,  $h_{fe} = 100$  and  $h_{oc} = 25 \mu\text{A/V}$ . It is used as an emitter follower amplifier with  $R_s = 1 \text{ K}\Omega$  and  $R_L = 5 \text{ K}\Omega$ . Determine for the amplifier  $A_{v_s} = v_o/v_s$ ,  $R_i$  and  $R_o$ . 5
- (b) For the two stage feedback amplifier shown in figure 1.0, determine the voltage gain  $A_{v_j} = v_o/v_s$ ,  $R_{if}$  and  $R_{of}$ . Assume that the transistors are identical and have  $h_{ie} = 2 \text{ K}\Omega$ ,  $h_{fe} = 80$  as parameters. 5

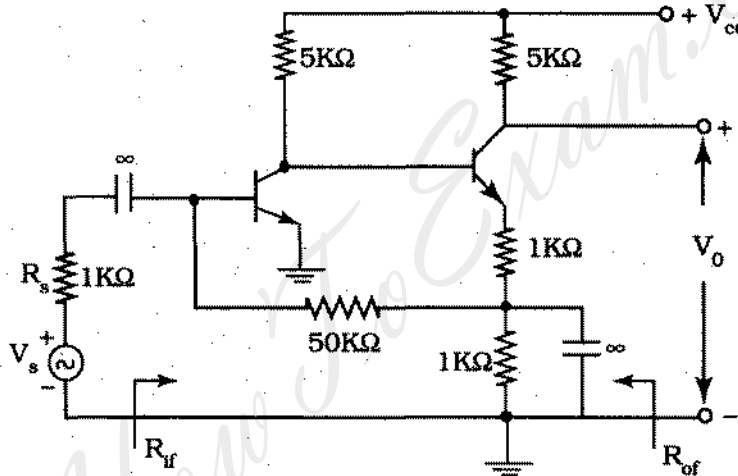


Figure 1.0

7. (a) What is a flyback converter? What are its advantages? Show the circuit diagram of a voltage regulator with fly back and explain its operation. 4
- (b) Draw the circuit diagram of a tuned class C power amplifier and explain its operation with waveforms. Give the complete analysis of the amplifier and derive the expression for its output power and collector circuit efficiency. 6