

**FACULTY OF ENGINEERING**

**B.E. II/IV Year (ECE) I Semester (Supplementary) Examination, April 2006**

**ELECTRONIC DEVICES**

Time : 3 Hours]

[Max. Marks : 75

Answer **all** questions in Part A and any **five** questions from Part B.

Assume reasonable values of data wherever necessary.

**Part A – (Marks: 25)**

1. Define the term current density  $J$ . What is the expression for  $J$  in terms of electron density and velocity? 3
2. Define 'ripple factor' and % regulation in rectifiers. 2
3. Explain the term thermal 'runaway'. 3
4. What are the differences between MOSFET and JFET? 2
5. What are the differences between light emitting diode and liquid crystal display? 3
6. Compare CC and CE configuration of transistor. 3
7. How UJT can be used as a relaxation oscillator? 3
8. Explain gain bandwidth product of BJT and FET. 2
9. In the case of collector to base bias circuit, if  $\beta = 40$ ,  $R_c = 4.7 \text{ k}\Omega$  and  $R_b = 80 \text{ K}\Omega$ , determine the value of stability factor  $S$ . 2
10. If  $\alpha$  of a BJT is 0.99, determine its value of  $\beta$ . 2

**Part B – (Marks:  $5 \times 10 = 50$ )**

11. (a) Derive the expression for the trajectory of an electron in uniform retarding field, when the initial velocity is making an angle ' $\theta$ ' with the field. 5
- (b) A charged particle having thrice the charge and mass twice that of an electron is accelerated through a potential difference  $V_A$  of 50 volts, before it enters a uniform magnetic field of flux density  $B$  of magnitude  $0.02 \text{ webers/m}^2$  normally with the field find.
  - (i) The velocity of charged particle between entering the field.
  - (ii) Radius of the path
  - (iii) Time of one revolution. 5

12. (a) Explain the V-I characteristics of P-n junction diode. Derive the equation for diode current. 5
- (b) In a P-N junction Ge diode, find the value of the voltage for which the reverse current  $I_0$  will reach 75% saturation value at the room temperature. 5
13. (a) Derive the relation between  $\alpha$  and  $\beta$  parameters of CB and CE operated transistors. 5
- (b) Sketch the profiles of majority and minority carrier currents in the base of an NPN transistor. Explain the transistor action with the help of these profiles. 5
14. (a) Derive the relationship between  $I_{DS}$ ,  $I_{DSS}$  and  $V_{GS}$  in a JFET and plot the transfer characteristics. 5
- (b) Explain how JFET acts as a voltage variable resistor at low  $V_{DS}$  values. 5
15. (a) Draw the hybrid- $\pi$  equivalent circuit of CE transistor at high frequencies. Derive expressions for the feedback conductance  $g_{b'c}$  and output conductance  $g_{ce}$ . 5
- (b) A junction transistor is to operate at the following operating point  $I_{CQ} = 2\text{mA}$ ,  $V_{CEQ} = 20\text{V}$  and  $I_{BQ} = 20\mu\text{A}$ . The following values for this operating point are the specifications of the transistor.  $\beta_0 = 100$ ,  $f_T = 50\text{ MHz}$ ,  $c_{ob} = 3\text{pf}$ ,  $h_{ie} = 1.4\text{K}\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{oe} = 20\mu\text{ mhos}$ . Determine the hybrid- $\pi$  model parameters of the transistor. Assume that the operating temperature is  $300^\circ\text{K}$ . 5
16. (a) Draw the circuit of a bridge rectifier and compare its performance with a full wave rectifier circuit using a mains transformer with centre tapped secondary winding. 5
- (b) No load output voltage for a rectifier with L-section filter is  $2V_m/\pi$ . Mention whether it is used with HWR or an FWR circuit. 5
17. (a) Draw the biasing circuits of MOSFET and explain. 5
- (b) Draw the characteristics of a MOSFET and explain its modes and regions of operation. 5