

(REVISED COURSE)


(3 Hours)

[Total Marks : 100


- N.B.: (1) Question No. 1 is compulsory.  
 (2) Answer any four questions out of remaining six questions.  
 (3) Figures to the right indicates full marks.

*Handwritten:* Electrical Networks 2/6/09  
 20  
 MASTRI

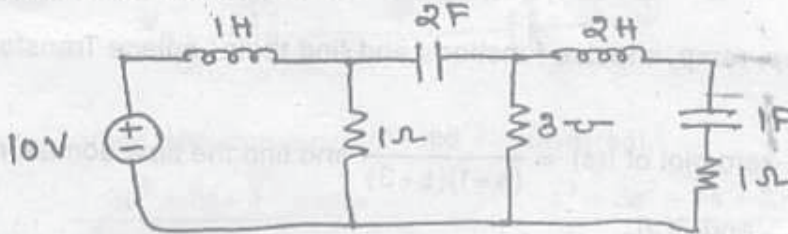
1. (a) Draw the dual of the network shown :



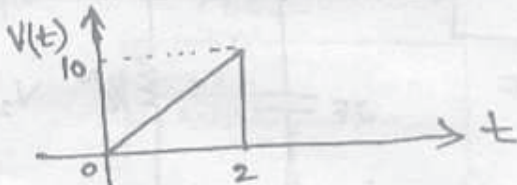
- (b) Test whether  $P(s) = s^6 + 8s^5 + 3s^4 + 15s^3 + 17s^2 + 12s + 4s$  is Hurwitz.  
 (c) Apply waveform synthesis and find Laplace transform for the following wave form.



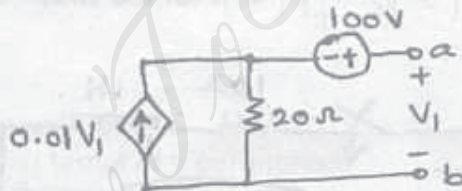
(d) Find Thevenin's equivalent voltage across a and b.



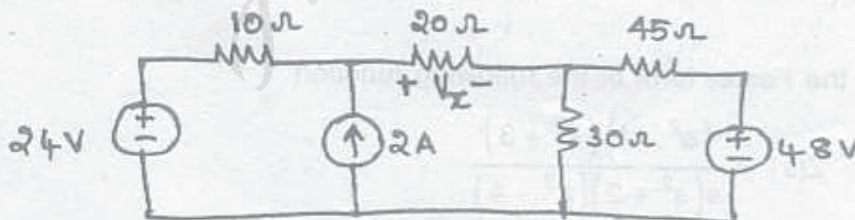2. (a) Use Superposition to find the value of  $V_x$  in the circuit shown. 10



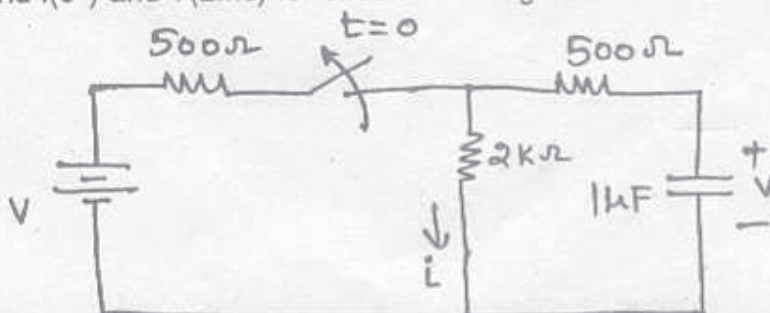
(b) Find  $i(0^+)$  and  $V(2ms)$  for circuit in the figure below : 10



[TURN OVER

Con. 2641-VR-3267-09

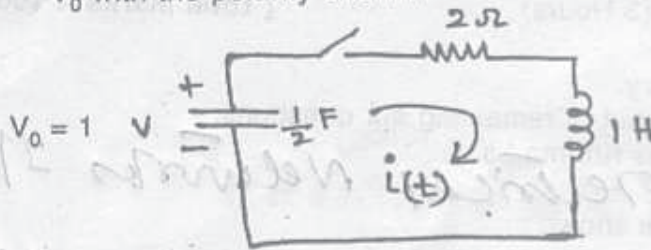
3. (a) Find  $i(t)$  using Laplace Transform. Given that capacitor is initially charged to  $10 V_0$  with the polarity shown.




- (b) Define step, ramp, impulse functions and find their Laplace Transforms. 10

4. (a) Draw pole-zero plot of  $I(s) = \frac{5s}{(s+1)(s+3)}$  and find the time domain response. 8

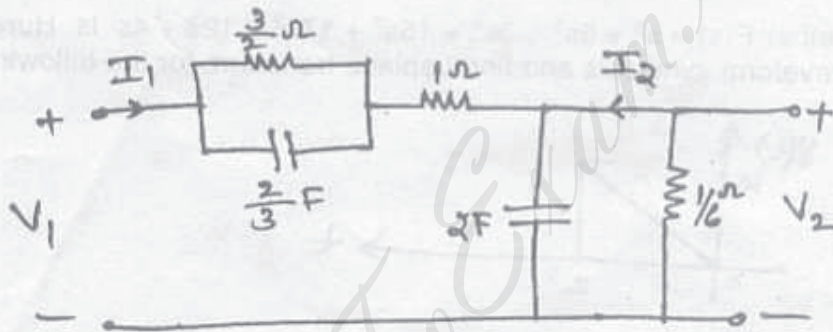- (b) Find  $V_2/V_1$  and  $I_1/I_2$ . 12



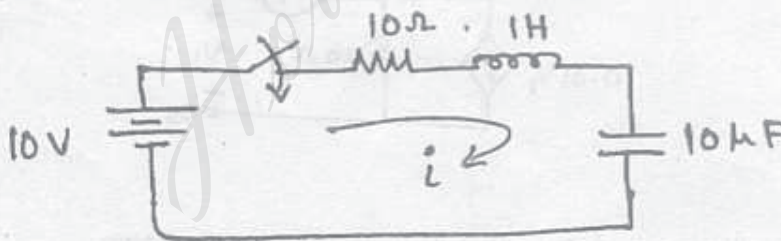5. (a) Find  $i(0^+)$ ,  $\frac{di}{dt}(0^+)$ ,  $\frac{d^2i}{dt^2}(0^+)$ , for the circuit shown.  $V_C(0) = 0$ . 10




- (b) Realize the Foster form of the following function 10

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$

Con. 2641-VR-3267-09.

Page 3.  
 3  
 3/6/08  
 Electrical Networks  
 10

6. (a) Find Z-parameters

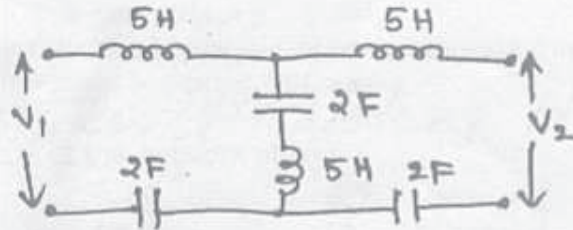

(b) Test whether following functions are Positive real.


10

(i)  $\frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$

(ii)  $\frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$

7. (a) Use nodal analysis to determine  $V_1$ .

10

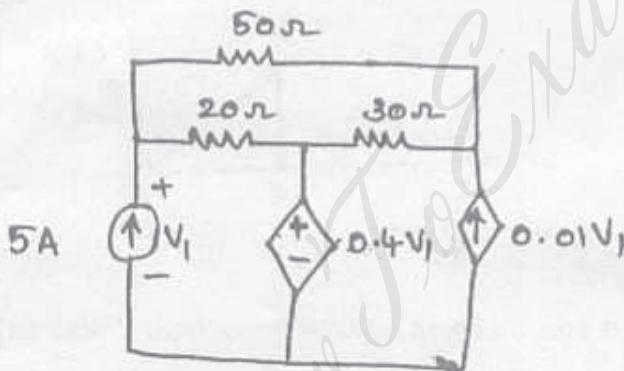

(b) Write short notes on any two :-

10

- (a) Z- parameters in terms of y parameters
- (b) Tellegen's and Millman's theorem.
- (c) Properties of RC function
- (d) Cut set matrix.