

T. E (E) ITRW
Power Electronics
(REVISED COURSE)

13/6/17
ND-1954

Con. 3356-07.

(3 Hours)

[Total Marks : 100

- N.B.(1) Question No. 1 is compulsory.
- (2) Answer any four questions from remaining six questions.
- (3) Assume additional suitable data wherever required.

T. E (E) ITRW Power Electronics 13/6/17

1. Answer any four :-

20

- (a) Draw and explain Gate characteristics of SCR.
- (b) Explain the triggering methods for an SCR
- (c) Compare properties of power BJT, power MOSFET and IGBT on application point of view.
- (d) Explain with neat diagram working principle of an inverter.
- (e) Explain how SCR is suitable than BJT, with suitable example.

- 2. (a) Sketch I-V characteristics of typical TRIAC. Explain its four quadrant operation. 10
- (b) Explain the buck regulator with help of circuit diagram and its waveform. Also derive the equation of output voltage. 10

- 3. (a) Draw and explain the circuit diagram for the synchronized UJT triggering with associated voltage waveform. Explain the necessity of synchronization. 10
- (b) Explain the different methods to achieve harmonic reduction in three phase inverters. 10

- 4. (a) Draw circuit diagram of Parallel inverter driving highly inductive load. Explain its feedback mode of operation. 10
- (b) Explain constructional features and working principle of IGBT. Give applications of IGBT. 10

- 5. (a) Draw a neat circuit diagram of one quadrant controlled bridge rectifier and explain its working. Draw the waveforms for— 10
 - (i) Supply voltage
 - (ii) Load current
 - (iii) Load voltage for $\alpha = 45^\circ$
 - (iv) Source current.
 consider continuous load current.

- (b) Explain the importance of isolation in gate drive circuits. 10

- 6. (a) Single phase full-bridge inverter has a resistive load $R = 3 \Omega$ and the d.c. input voltage $E_{dc} = 50 V$. Calculate : 10

- (i) the RMS output voltage at the fundamental frequency
- (ii) the output power (p_o)
- (iii) Average and peak currents of each thyristor
- (iv) Peak reverse-blocking voltage of each thyristor.

- (b) Draw the circuit for 1 ϕ AC regulator and explain its operation with appropriate waveforms. 10

- 7. (a) Draw the circuit diagram of Jone's chopper and explain its working in details with relevant waveforms. 12

- (b) Compare Morgan chopper with Jone's chopper 5

- (c) Give and explain in short any two applications of chopper circuit. 3