

Library

VE Nov 07 29

T.E. (Elect) (Sem.VI) (Rev).
Power Electronics

9/12/07

Con/5530-07.

(REVISED COURSE)
(3 Hours)

CD-5523

[Total Marks : 100

- N.B. : (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions from remainings questions.
 (3) Assume **suitable** data wherever **necessary**.

Master

1. (a) Explain the following ratings of SCR – 10
 - (i) I^2t rating
 - (ii) di/dt rating
 - (iii) Holding and latching current
 - (iv) Peak inverse voltage
 - (v) dv/dt rating.
- (b) (i) Compare properties of power BJT, MOSFET and IGBT from application point of view. 5
- (ii) Explain protection methods used for over current, overvoltage, dv/dt and di/dt . 5
2. (a) Draw a three phase full bridge inverter using SCR and its waveform for 120° conduction and 180° conduction. Explain operation in brief. 10
- (b) Describe different commutation techniques used in case of SCR. 10
3. (a) Draw and explain circuit diagram for synchronized UJT triggering with associated waveforms. Also explain necessity for synchronization. 10
- (b) Explain with the help of neat diagram, construction and operating principle of IGBT. 10
4. (a) Sketch I-V characteristics of typical TRIAC. Explain it's four quadrant operation and compare it with SCR. 10
- (b) What are different methods to reduce harmonics in 3ϕ inverter? Explain briefly. 10
5. (a) Draw circuit diagram of single phase A.C. regulator for R-L load using phase control. Give waveform of input, output voltage and currents. 10
- (b) Derive the expressions for RMS value of output voltage and current for the above circuit. 10
6. (a) Draw circuit diagram of multiple pulse PWM single phase inverter and explain its working with suitable waveforms. Give advantages of PWM Technique. 10
- (b) Explain basic operation of SCR with suitable circuit diagram. Also write difference between SCR and BJT. 10
7. (a) Draw the circuit diagram of Jone's chopper and explain its working in detail with relevant waveforms. 12
- (b) Compare Morgen chopper with Jone's chopper. 8
