

BACHELOR OF SCIENCE (B.Sc.)

Term-End Examination

December, 2005

PHYSICS

**PHE-10 : ELECTRICAL CIRCUITS AND
ELECTRONICS**

Time : 2 hours

Maximum Marks : 50

Note : Question no. 1 is **compulsory**. Attempt any **four** questions from the rest. Use of log tables and non-programmable calculators is allowed. Symbols have their usual meanings.

1. Attempt any **five** parts.

- (a) Differentiate between lumped and distributed elements. Give one example of each. 2
- (b) What do you understand by non volatile memories ? 2
- (c) Define rise time and fall time of a signal. 2
- (d) Why is D-latch called a transparent latch ? 2
- (e) Define ripple factor and give its physical significance. 2
- (f) Why is operational amplifier also called a comparator ? 2

2. (a) State and prove reciprocity theorem. 2+2
- (b) Draw the circuit diagram of a Wien-Bridge oscillator. Explain its working and write down the expression for output frequency. 6
3. (a) Draw and explain the $I - V$ characteristics of a $p - n$ junction with external voltage. 5
- (b) Design a T-pad attenuator to give an attenuation of 80 dB and to work on a line of 100Ω impedance. 5
4. (a) Explain with the help of a suitable diagram how the two stages of an amplifier are coupled using a resistance and a capacitor. How does this coupling affect the frequency response ? 5
- (b) In a centre tap full wave rectifier, the load resistance, $R_L = 1.2 \text{ k}\Omega$. Each diode has a forward-bias dynamic resistance r_d of 8Ω . The voltage across half the secondary winding is $220 \sin 314 t$. Find the peak value, dc value, the rms value of the current, ripple factor and rectification efficiency. 5
5. (a) Using IC 741 C operational amplifier draw the circuit diagram of the basic differentiator and obtain an expression for the output voltage. 5
- (b) Using an IC LM 317, design an adjustable voltage regulator for an output voltage of 5 V to 18 V. 5

6. (a) Convert decimal 872 to its BCD (8421) code equivalent. 2
- (b) Simplify the Boolean expression
$$Z = (B + \bar{C})(\bar{B} + C) + \overline{(\bar{A} + B + \bar{C})}$$
 3
- (c) Design a MOD-6 counter using JK flip-flop and explain its working. 5
7. (a) Explain the concept of feed-back in an op-amp with the help of a suitable diagram. What do you understand by positive and negative feed-backs? List one application of each. 5
- (b) Explain the working of a cathode ray oscilloscope with the help of a block diagram. List two of its applications. 5