

(EM 314)

III/IV B.Tech. DEGREE EXAMINATION, OCTOBER 2005.

First Semester

VHDL

Time : Three hours

Maximum : 70 marks

Answer Question No.1 compulsorily. (7 × 2 = 14)

Answer ONE question from each Unit. (4 × 14 = 56)

All questions carry equal marks.

1. (a) What is a typical design flow for designing VLSI IC circuits?
- (b) Difference between top – down and bottom – up design methodologies for digital design.
- (c) What are the logic value set and data types such as any nets, registers and numbers?
- (d) Explain the port connection rules in a module instantiation.
- (e) What are fall and turn-off delays in the gate-level design?
- (f) Enumerate the continuous assignments (assign) statement and restrictions on the assign statement.
- (g) Give the significance of structured procedures always and initial in behavioral modeling.

UNIT I


2. (a) Explain the following basic VHDL building blocks :
  - (i) Entity
  - (ii) Architecture
  - (iii) Configuration
  - (iv) Driver.

Or

- (b) Write the following variables in VHDL.
  - (i) An 8-bit vector net called a\_in.
  - (ii) A 32-bit storage register called address. Bit 31 must be the most significant bit. Set the value of the register to a 32-bit decimal number equal to 3.
  - (iii) A time variable called snap\_shot.
  - (iv) A memory MEM containing 256 words of 64 bits each.

UNIT II

 3. (a) Describe how signal assignments are the most basic form of VHDL with suitable examples. A 4-bit parallel shift register has I/O pins as shown in the figure below. Write the module definition for this module shift\_reg. Include the list of ports and port declarations. You do not need to show the internals.



Or


- (b) Explain how subprograms consist of functions and procedures with examples.
- (c) Describe how functions can be used as resolution functions to calculate the proper value on a multiple driven or iterative network.

UNIT III

4. (a) With the help of suitable examples, explain how types can be used by three different types of objects: the signal, variable and constant. Explain how enumerated types can be used to describe user-defined operations and make a model much more readable.

Or

 (b) Design a 2-to-1 multiplexer using bufif0 and bufif1 gates as shown below :



Assume suitable delay specification for gates b1 and b2. Apply stimulus and test the output values.

UNIT IV

5. (a) A full subtractor has three 1-bit inputs x,y and z (previous borrow) and two 1-bit outputs D(difference) and B(borrow). The logic equations for D and B are as follows :

$$D = x'.y'.z + x'.y.z' + x.y.z' + x.y.z$$

$$B = x'.y + x'.z + y.z$$

Write the full VHDL description for the full subtractor module, including I/O ports (Remember that + in logic equations corresponds to a logical or operator in dataflow). Instantiate the subtractor inside a stimulus block and test all eight possible combinations of x, y and z given in the following truth table.

X	Y	Z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Or

(b) Design a negative edge-triggered D-flip-flop (D\_FF) with synchronous clear, active high D\_FF clears only at a negative edge of clock when clear is high). Use behavioral statements only. (Hint : Output q of D\_FF must be declared as reg). Design a clock with a period of 10 units and test the D-FF.